

# Transistors



# Course Content

Transistors:

Transistor configurations: CB, CE and CC; Transistor parameters: alpha, beta and gamma, working of transistor as a switch, Amplifier.



# Bipolar Transistor Configurations

- At the end of this lecture, student will be able to :
  - Define transistor
  - Explain the working of transistor
  - Explain the transistor configurations
  - Draw the input output characteristics of BJT




# Topics


- Introduction
- An Overview of Bipolar Transistors
- Bipolar Transistor Operation
- Bipolar Transistor configurations
- Bipolar Transistor Characteristics





# Introduction to BJT

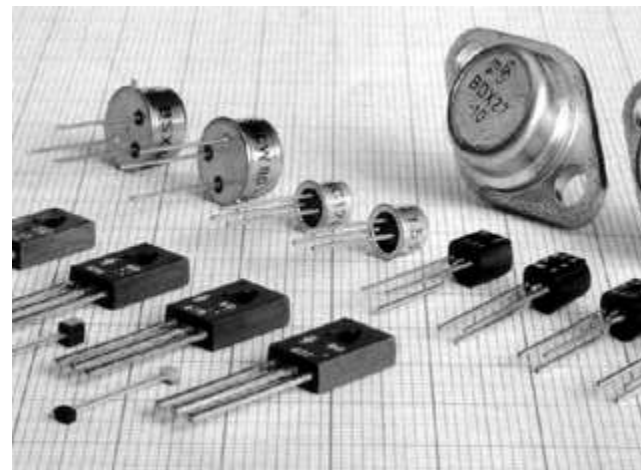

# Basic models of BJT

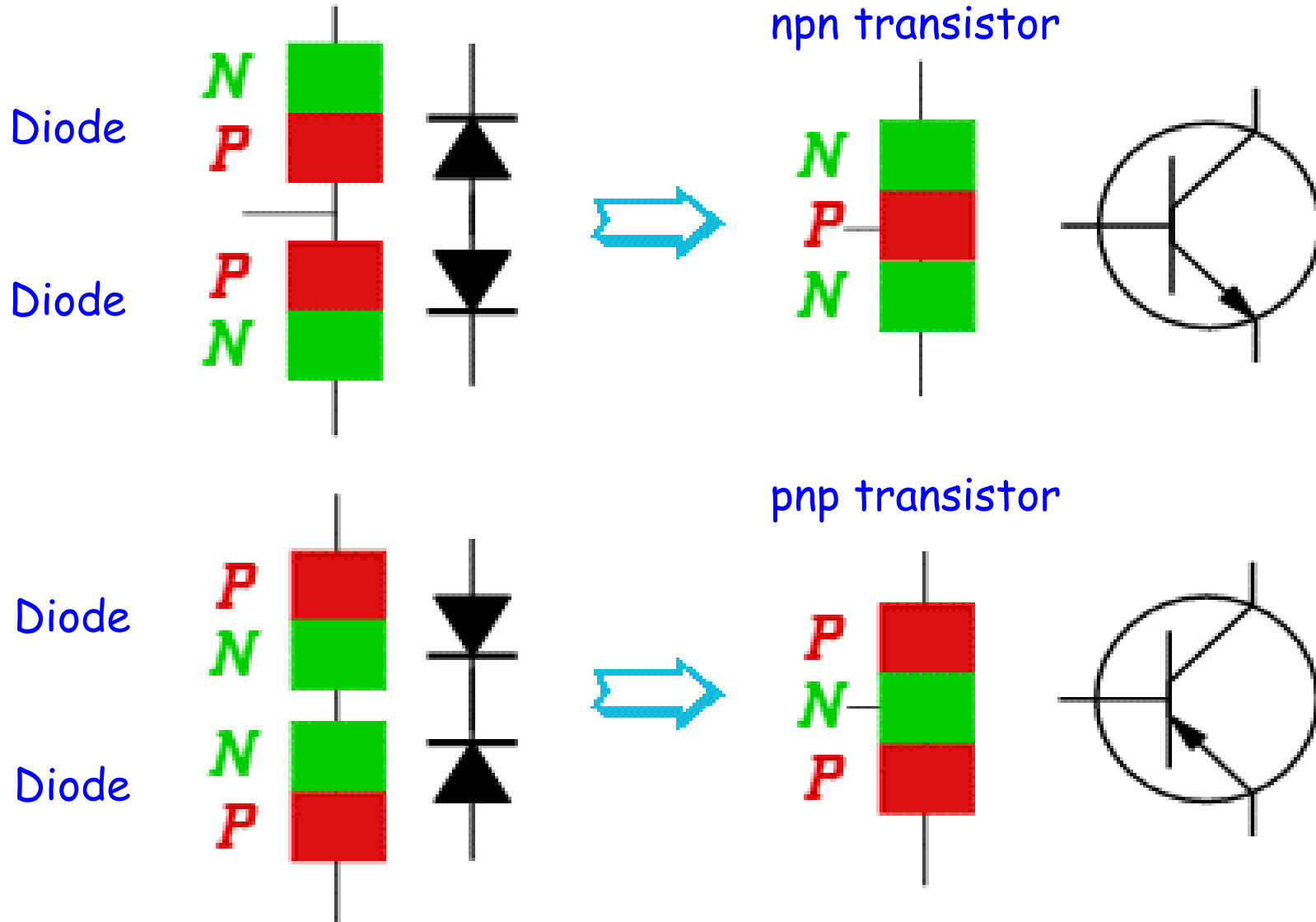


# Transistor Structure

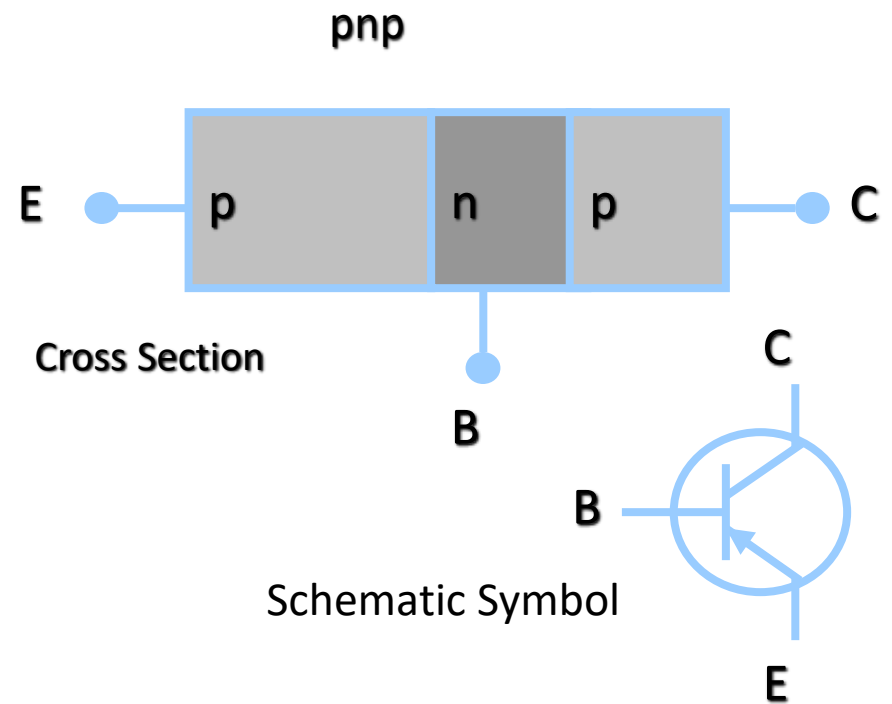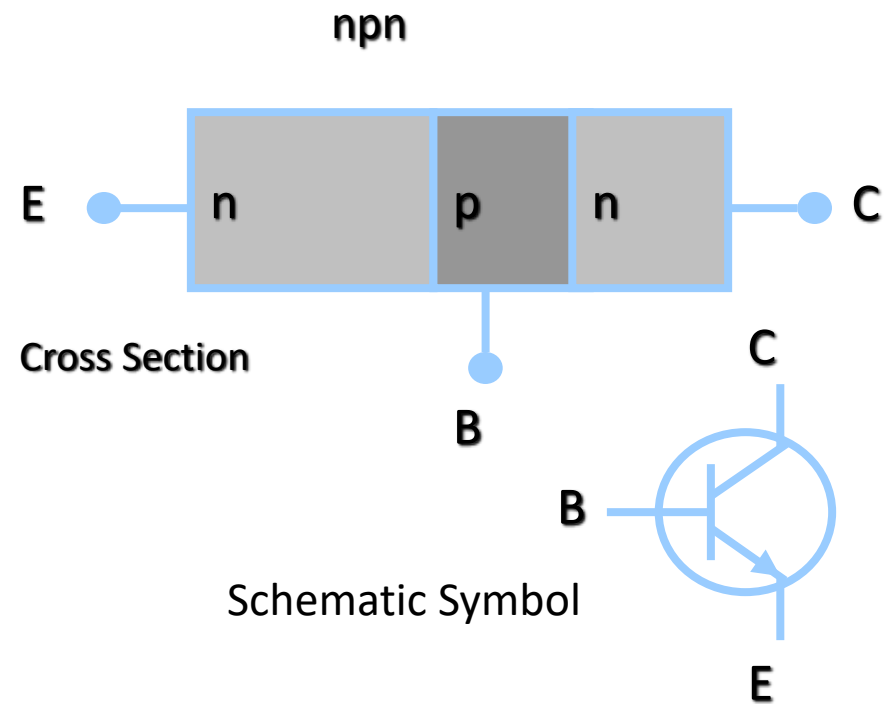

- Collector doping is usually  $\sim 10^9$
- Base doping is slightly higher  $\sim 10^{10} - 10^{11}$
- Emitter doping is much higher  $\sim 10^{17}$




# BJT Current and Voltage - Equations

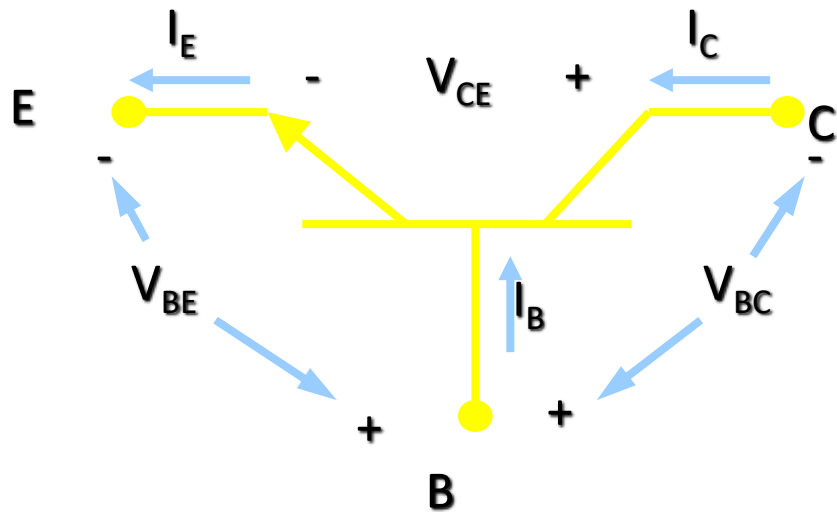

**npn**

$$I_E = I_B + I_C$$

$$V_{CE} = -V_{BC} + V_{BE}$$

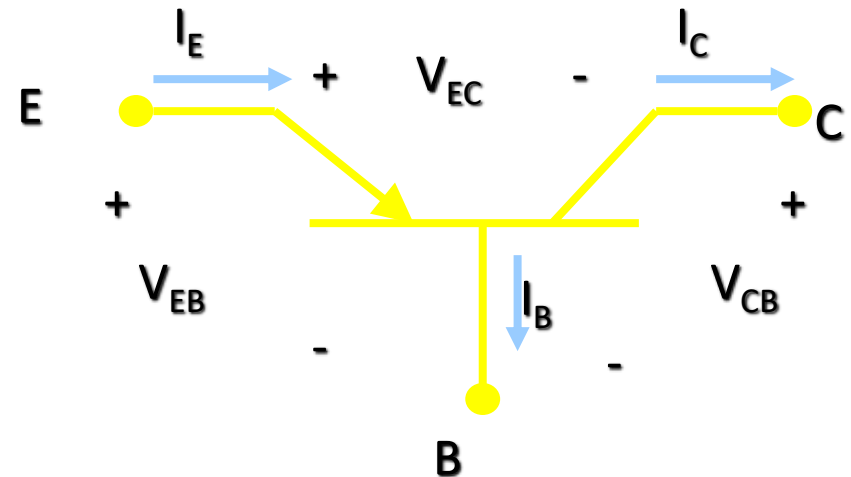

**pnp**


$$I_E = I_B + I_C$$

$$V_{EC} = V_{EB} - V_{CB}$$






# Understanding of BJT

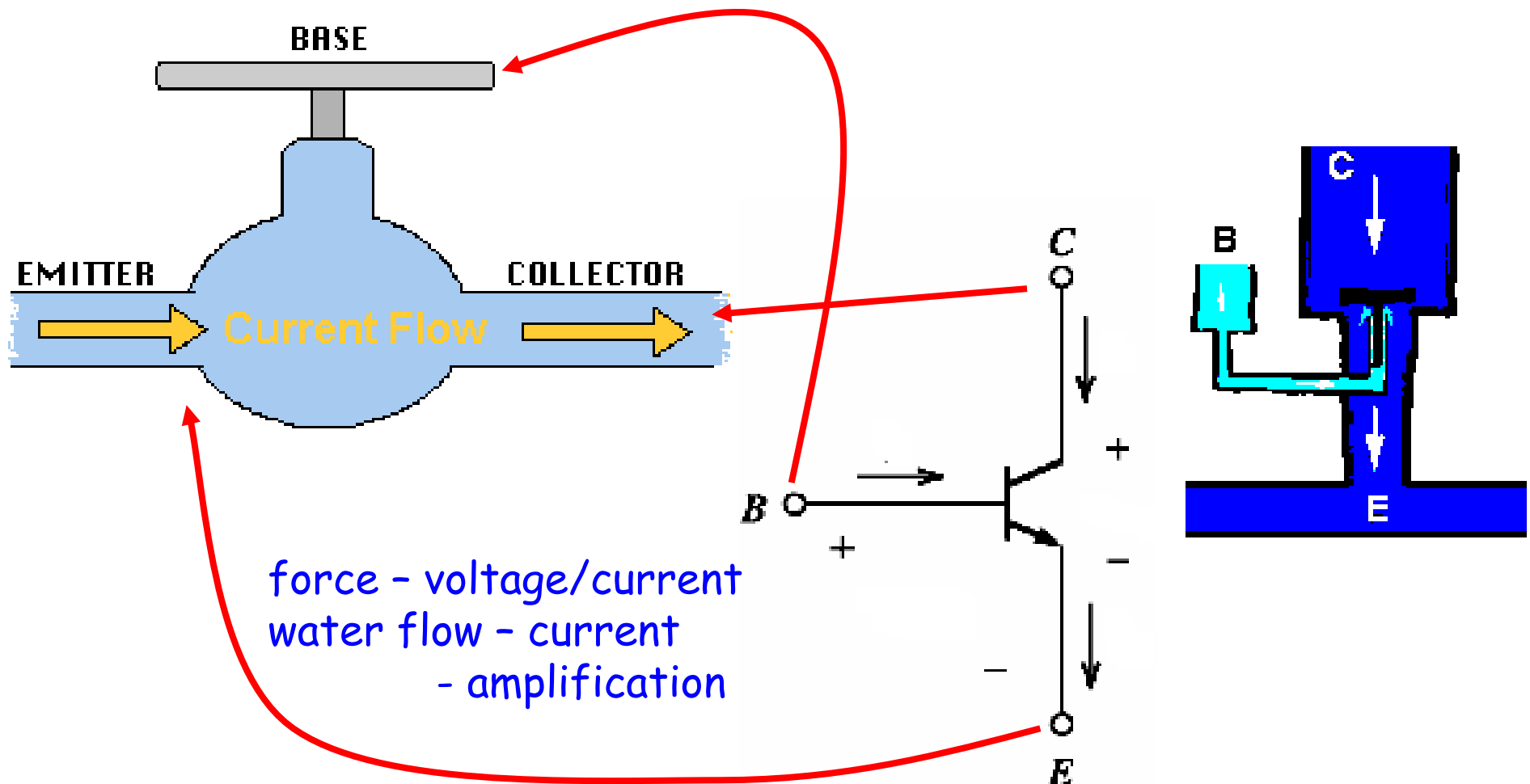


# BJT Operation

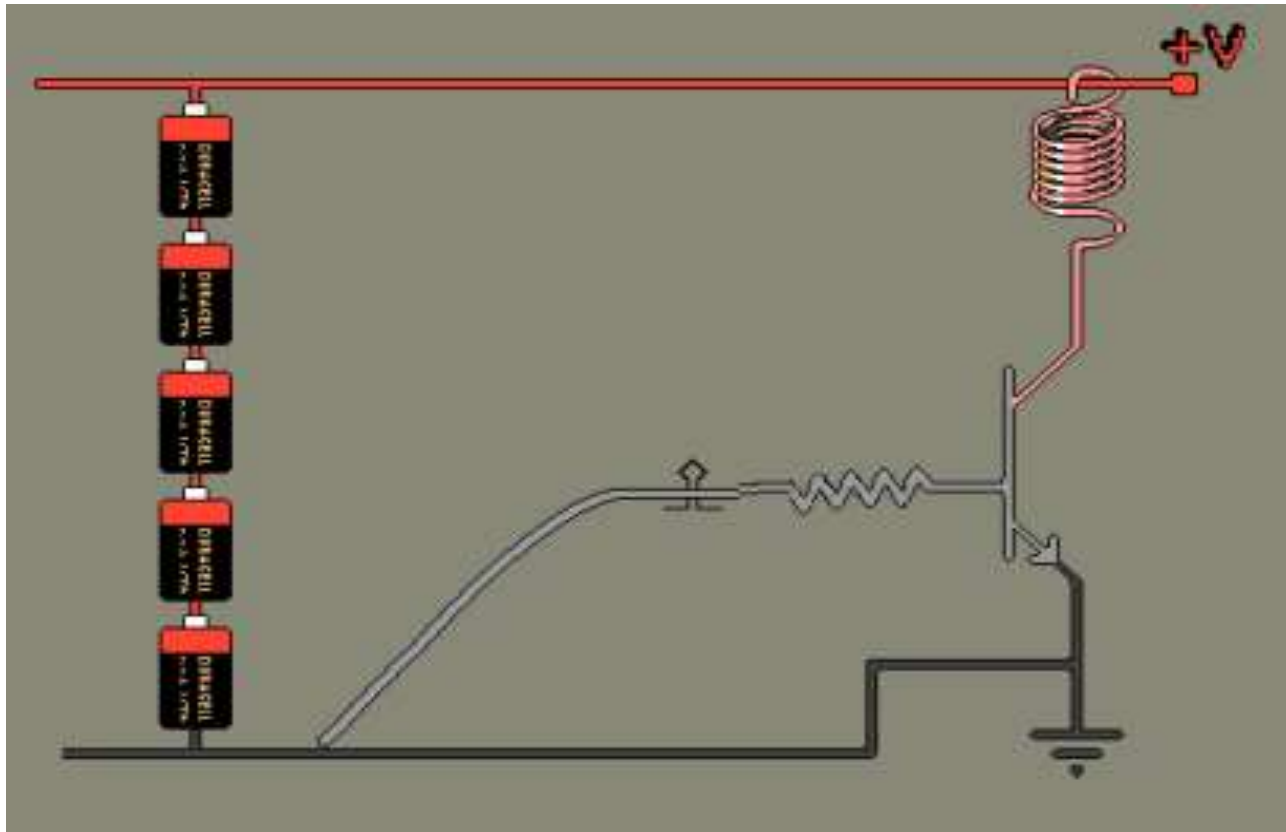

Voltage to current convertor in the base circuit

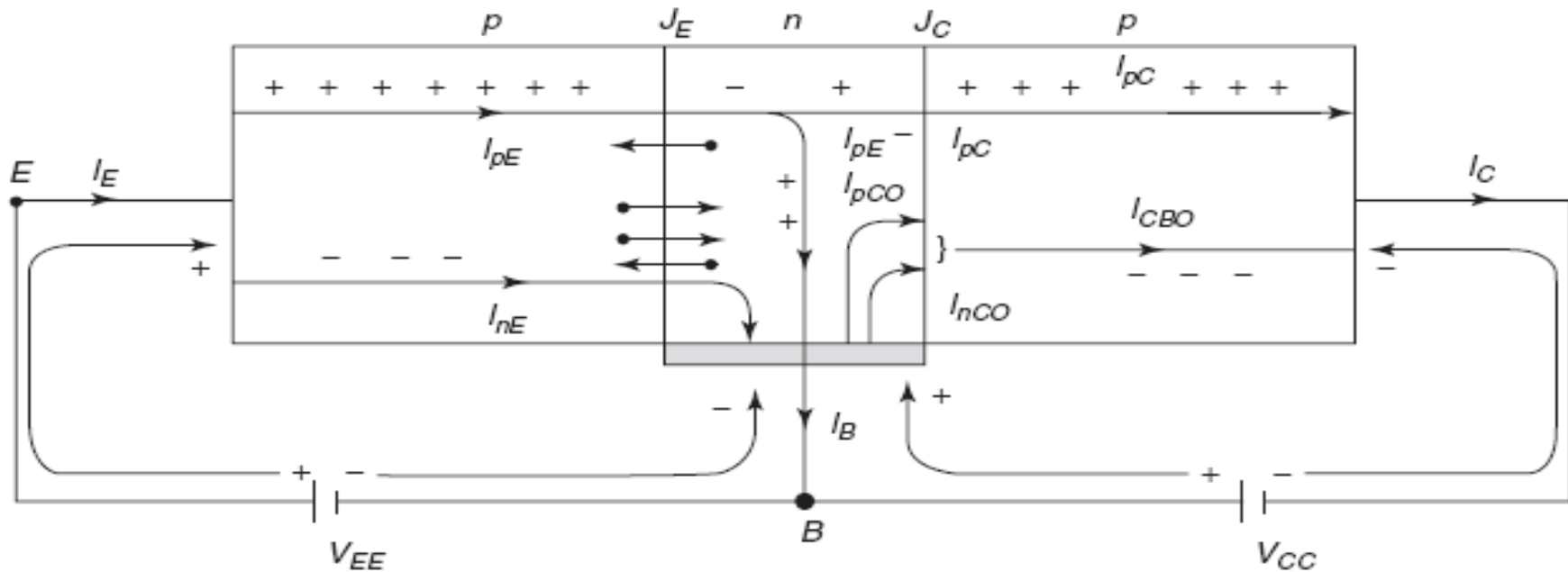
# Transistor Current Components

- Current Components in *p-n-p Transistor*




# Transistor Current Components continued..
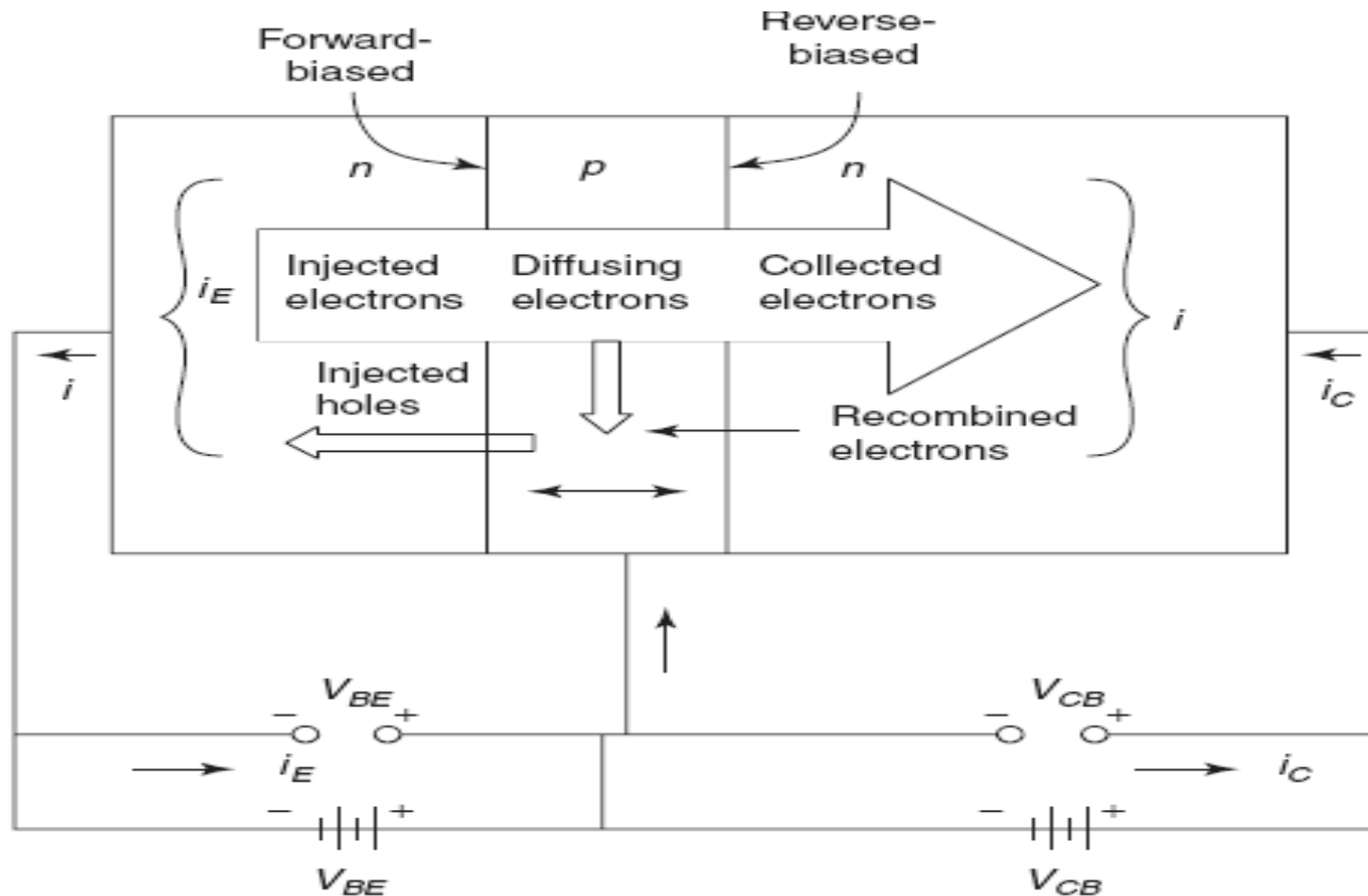
## ❖ Current Components in an *n-p-n* Transistor



# How Transistor Works

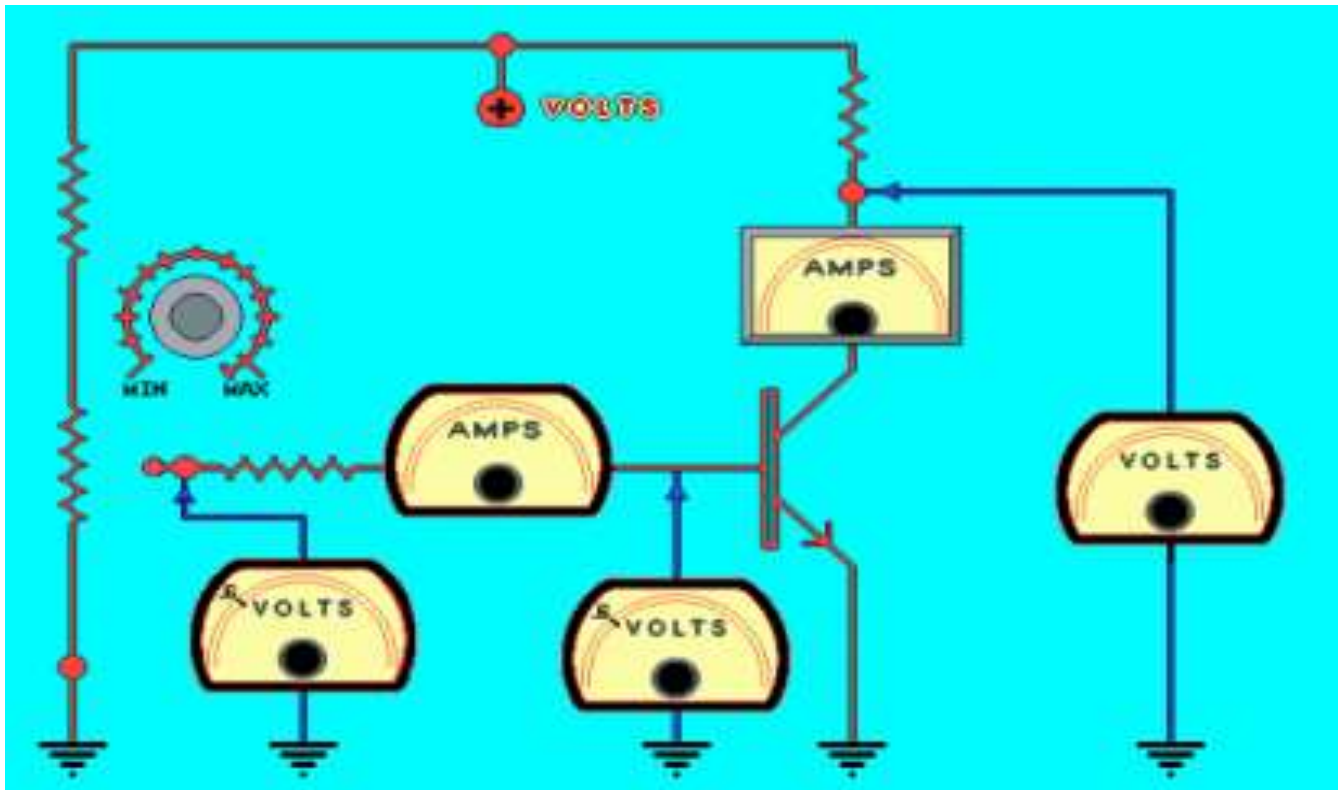


# Bipolar Transistor Operation


- Consider npn transistors
  - pnp devices are similar but with different polarities of voltage and currents
  - when using npn transistors
    - collector is normally more positive than the emitter
    - $V_{CE}$  might be a few volts
    - device resembles two back-to-back diodes – but has very different characteristics
    - with the base open-circuit negligible current flows from the collector to the emitter




# BJT configurations

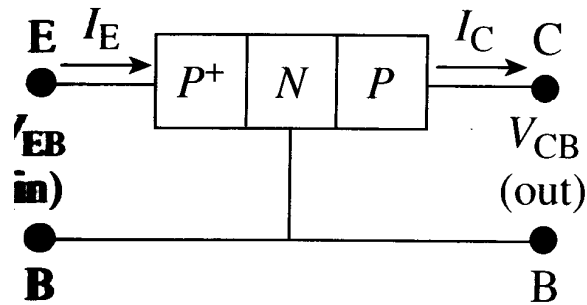

(a) Common base

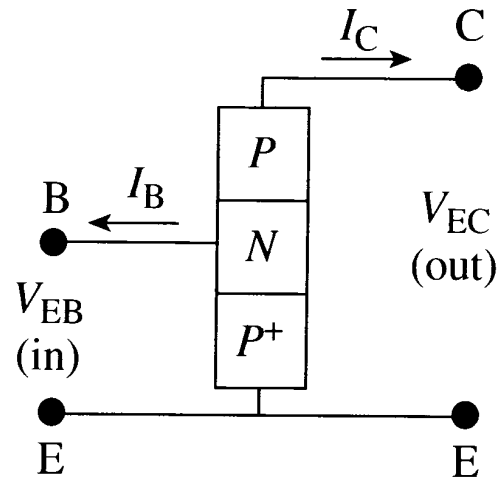

(b) Common emitter

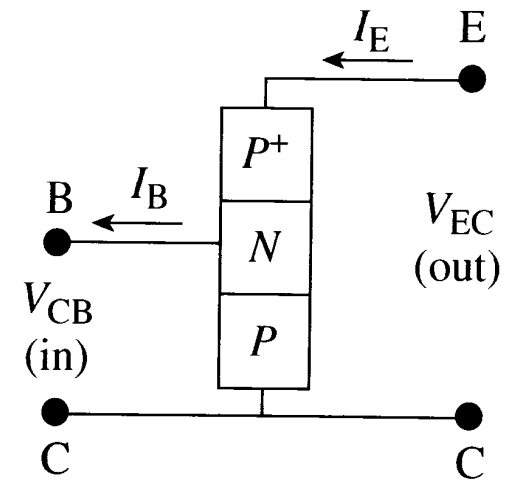

(c) Common collector



# BJT configurations Continued..

Biasing the transistor refers to applying voltages to the transistor to achieve certain operating conditions.

1. Common-Base Configuration (CB) :      input =  $V_{EB}$  &  $I_E$   
output =  $V_{CB}$  &  $I_C$

2. Common-Emitter Configuration (CE): input =  $V_{BE}$  &  $I_B$   
output =  $V_{CE}$  &  $I_C$

3. Common-Collector Configuration (CC) : input =  $V_{BC}$  &  $I_B$   
(Also known as Emitter follower)      output =  $V_{EC}$  &  $I_E$






# BJT Biasing Modes

<b>Bias Mode</b>	<b>E-B Junction</b>	<b>C-B Junction</b>
Saturation	Forward	Forward
<b>Active</b>	<b>Forward</b>	<b>Reverse</b>
Inverted	Reverse	Forward
Cutoff	Reverse	Reverse




# Transistor Characteristics

## Input Characteristics

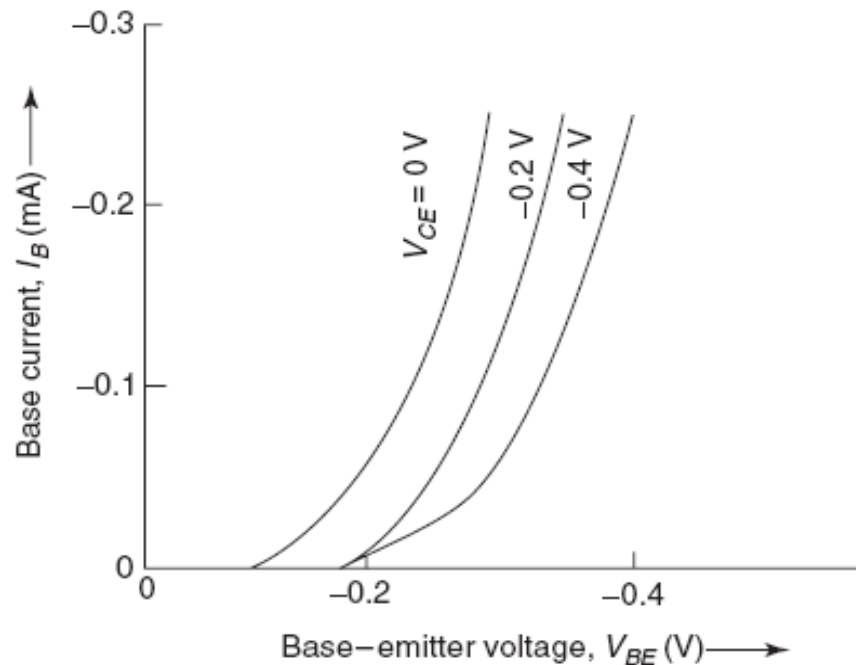



**Input characteristics in the CE mode**

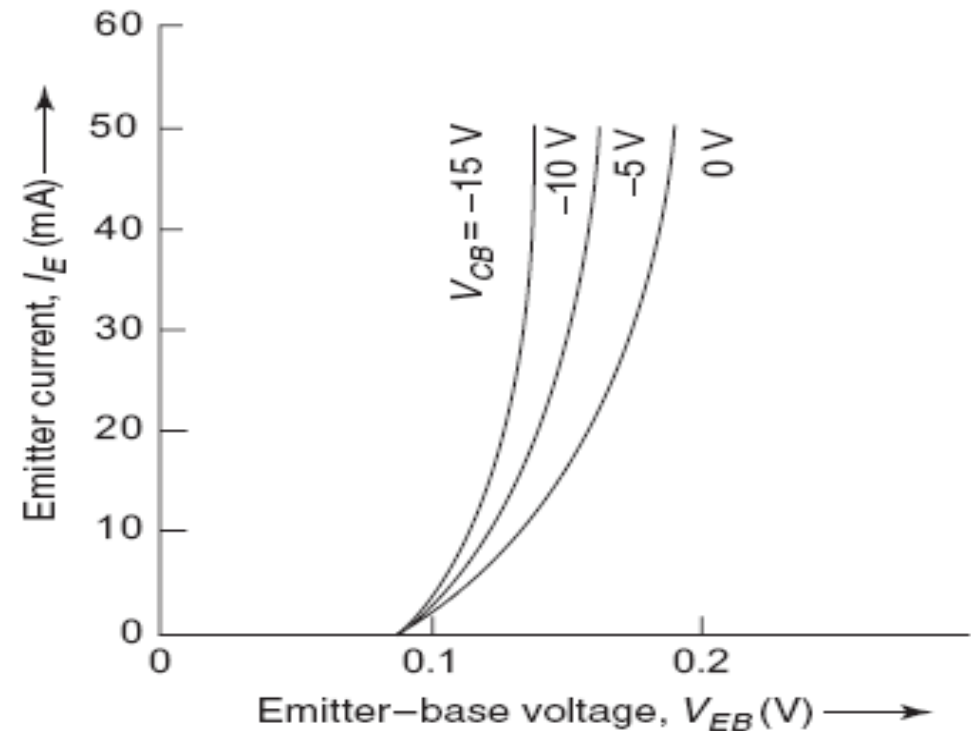


**Input characteristics in the CB mode**



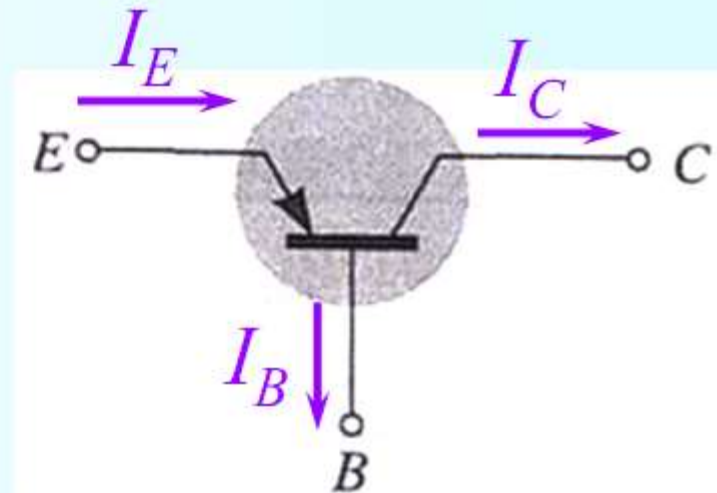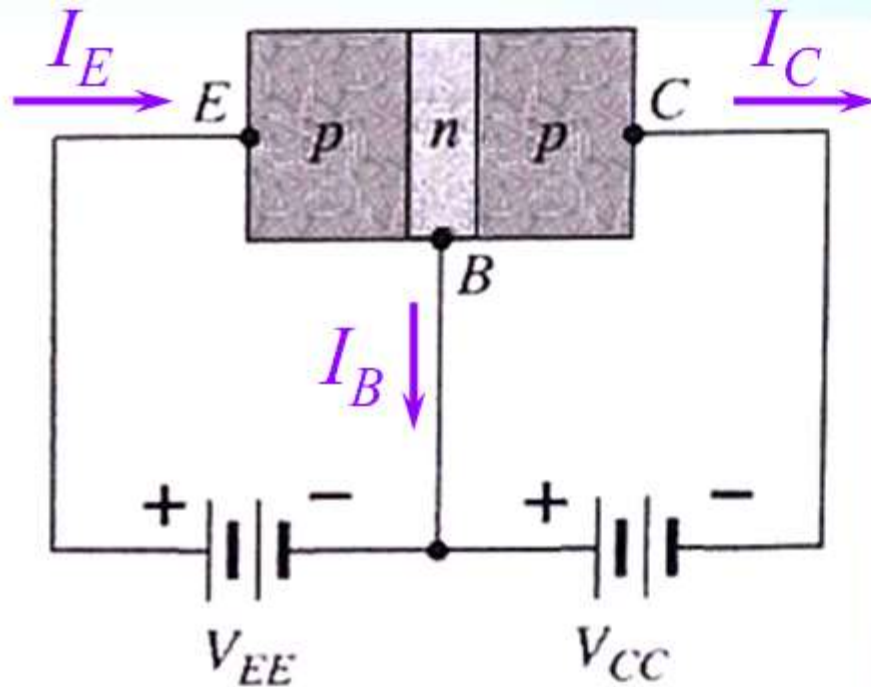
# Common-Base Configuration of pnp Transistor



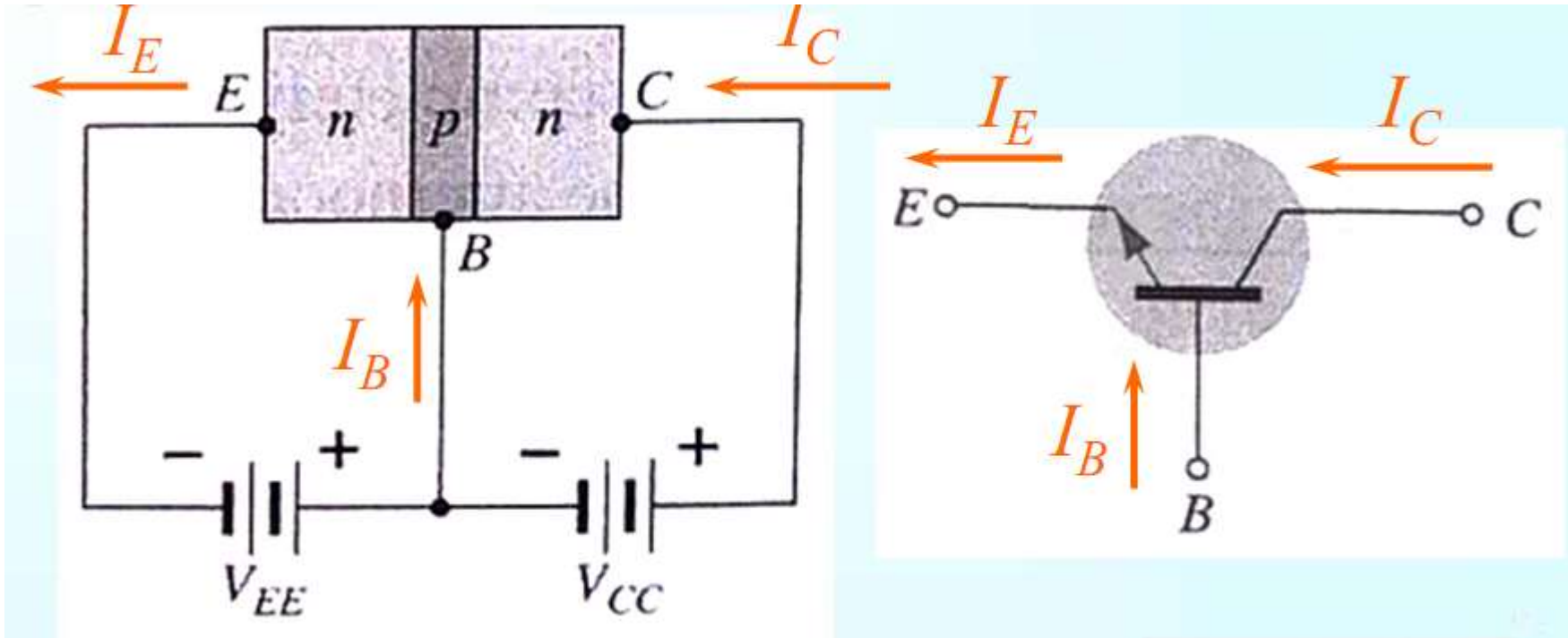
# Common-Base Configuration of npn transistor




# Common Base Input Characteristics

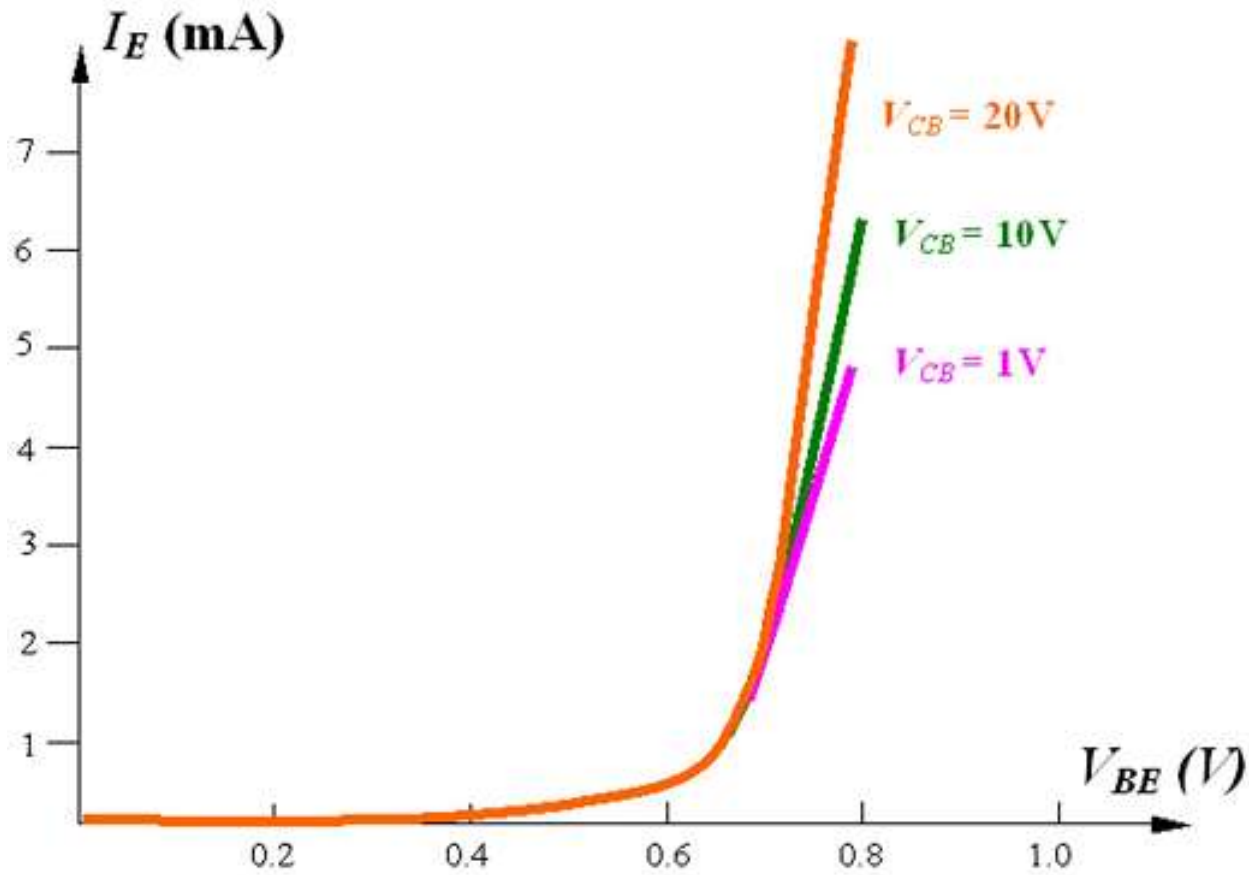


# Common Base Output Characteristics

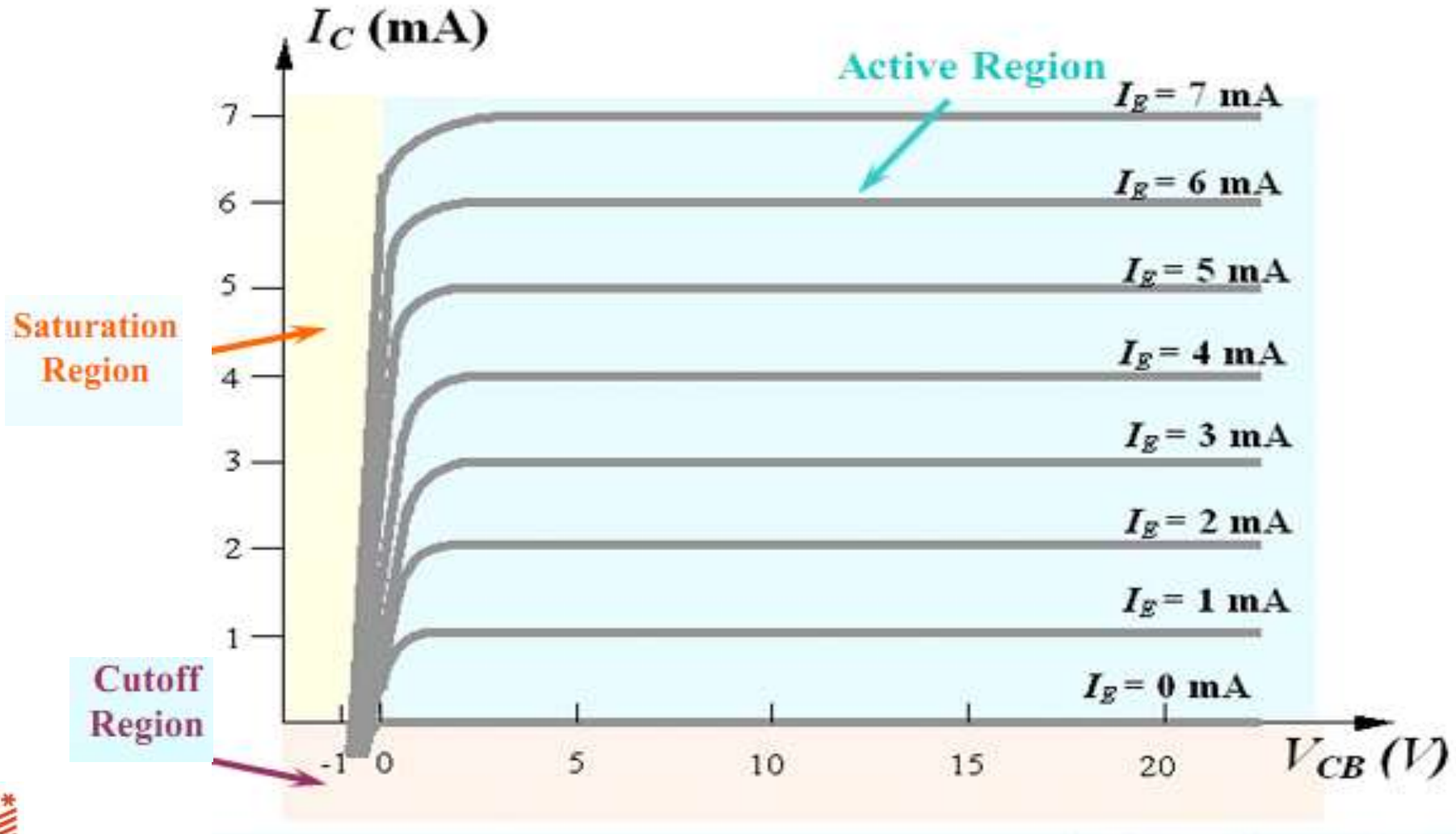
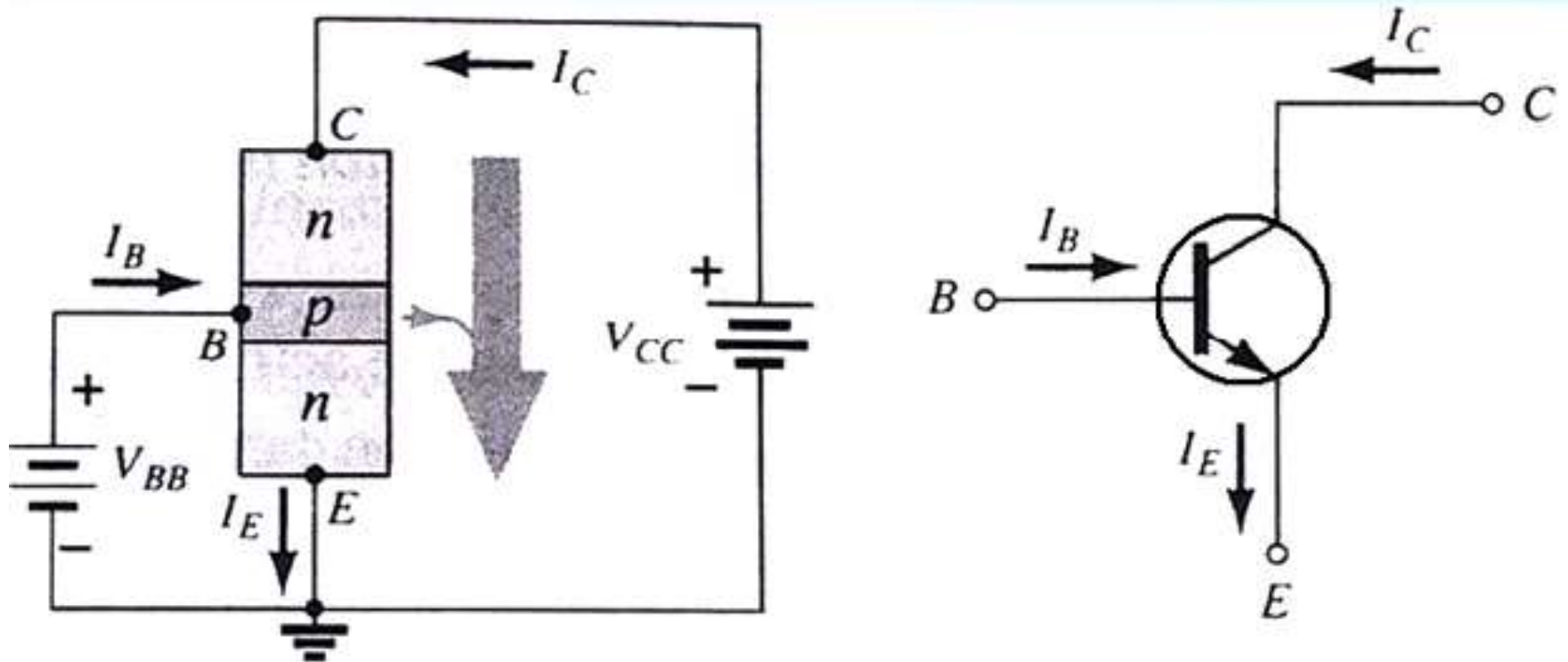
# Common-Emitter Configuration of npn Transistor



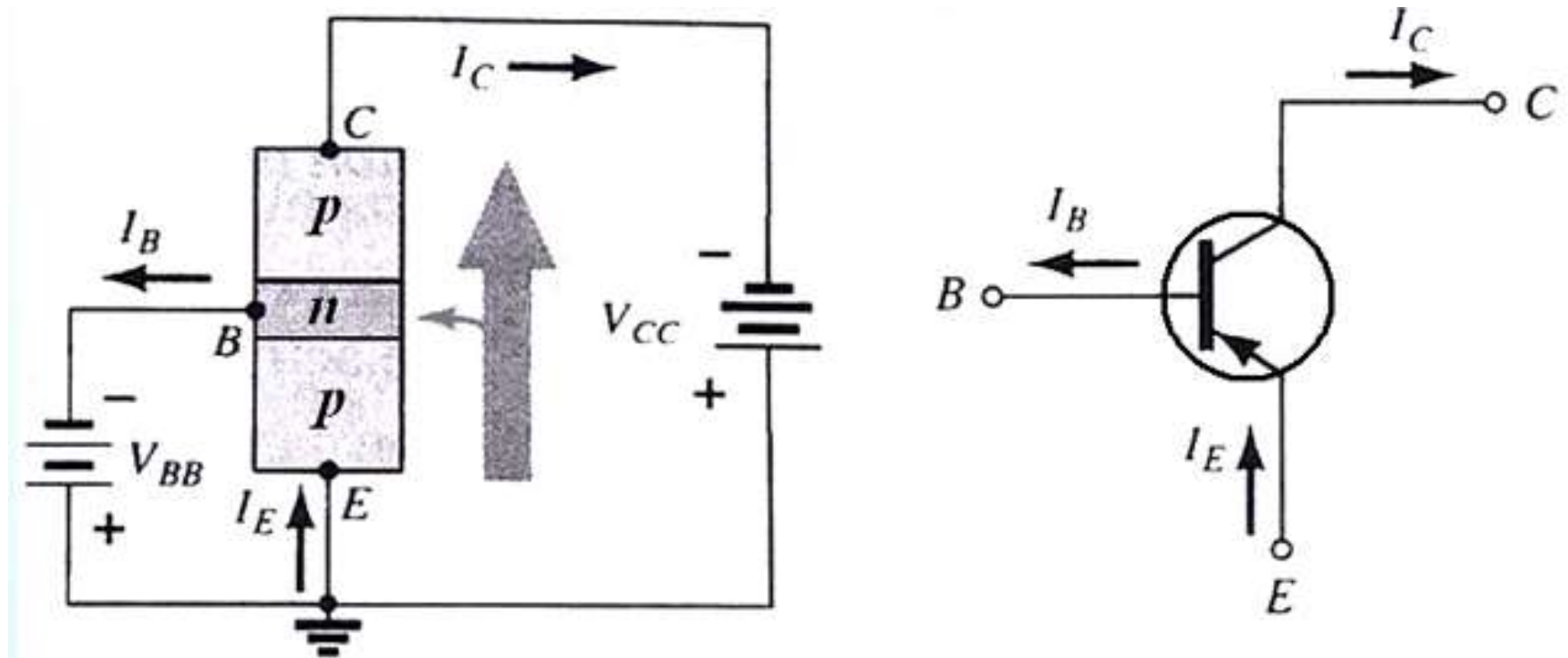
# Common-Emitter Configuration of pnp Transistor







# Common Emitter Input Characteristics

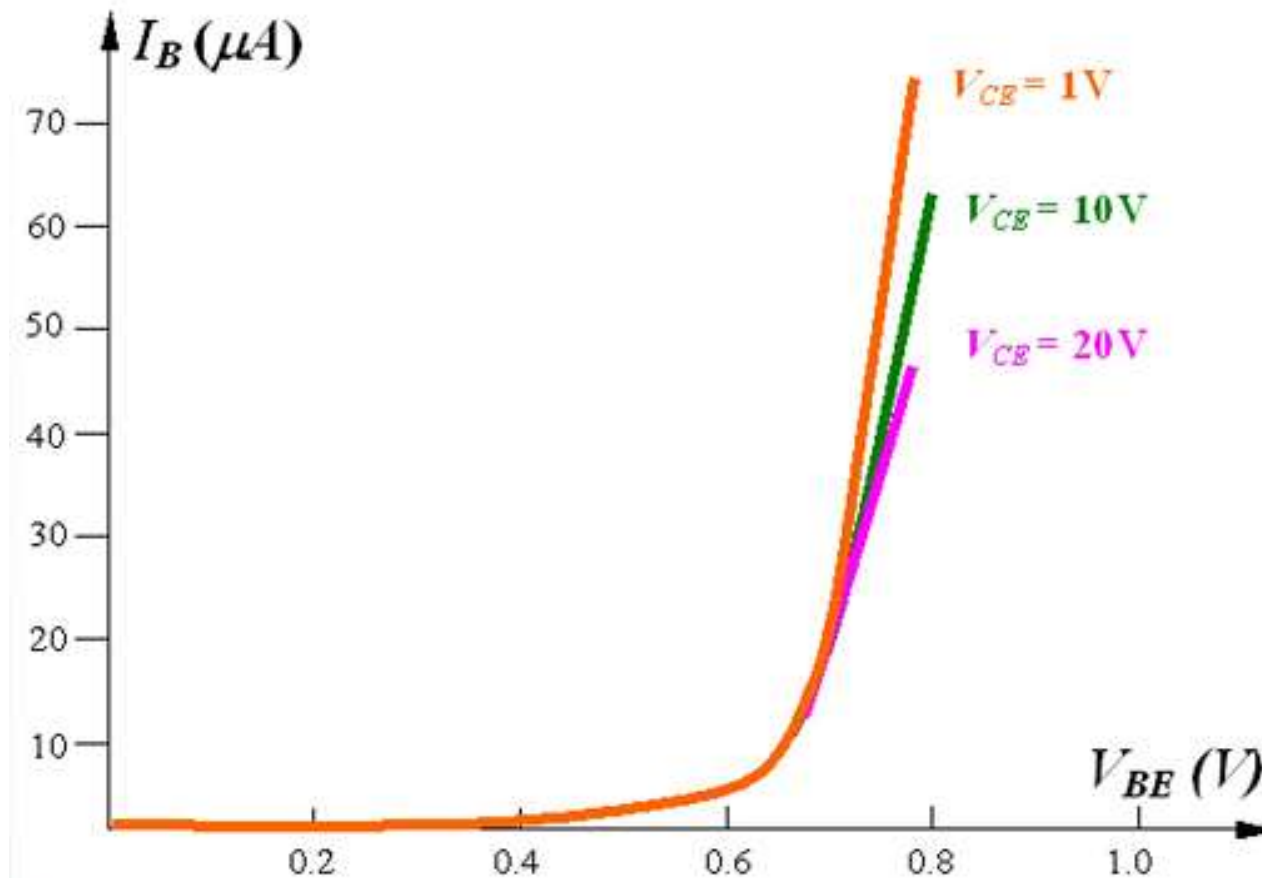


# Common Emitter Output Characteristics

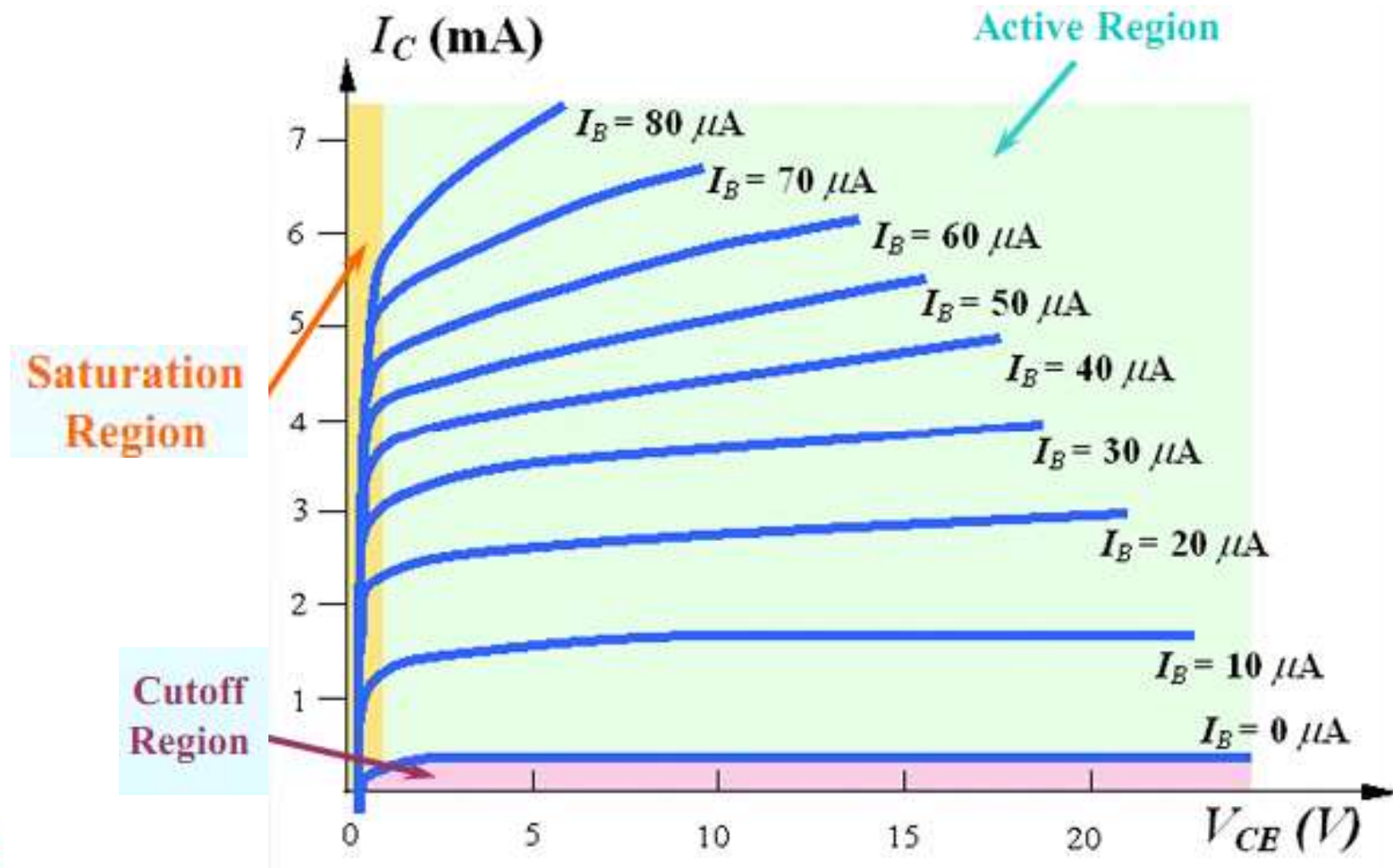

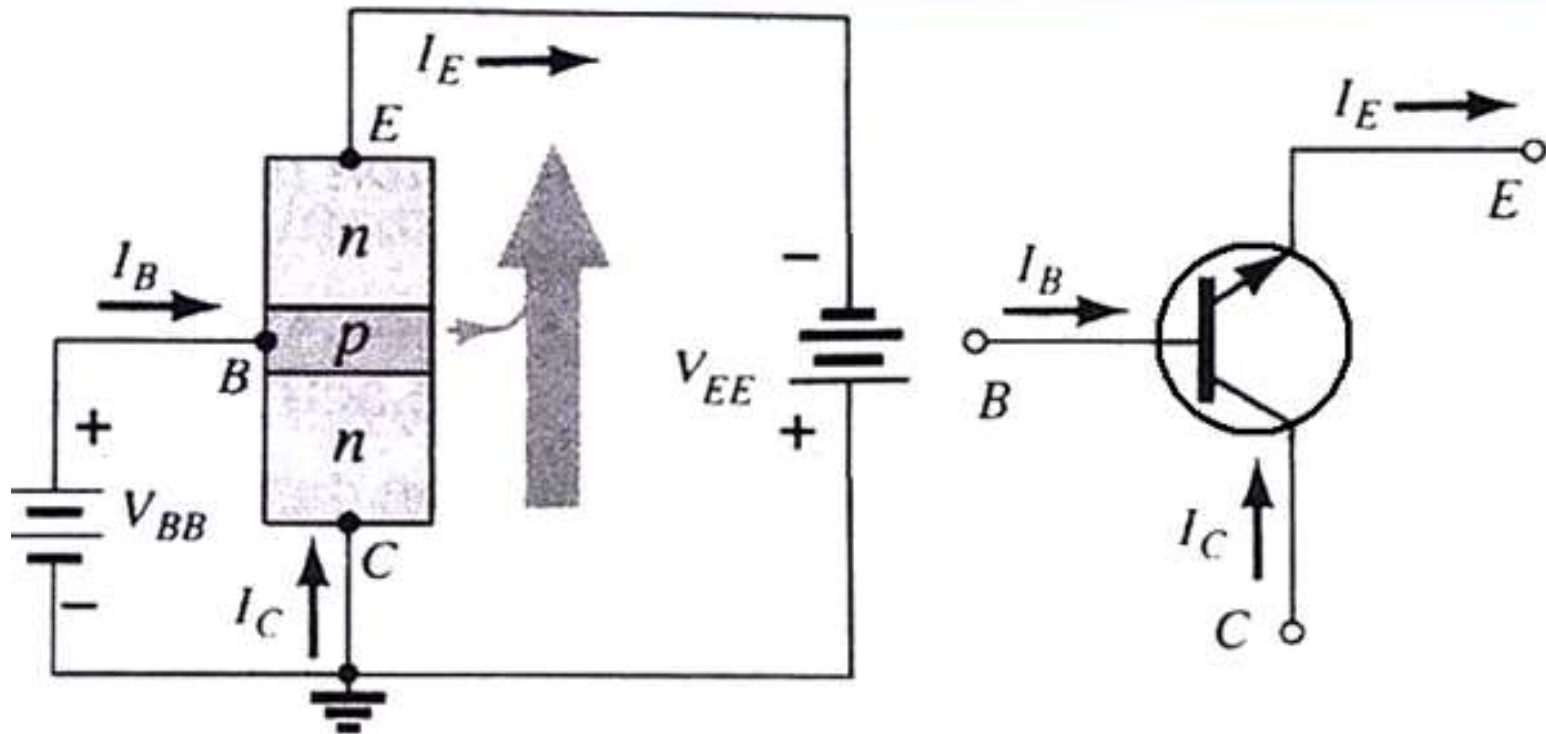
# Common-Collector Configuration of npn Transistor


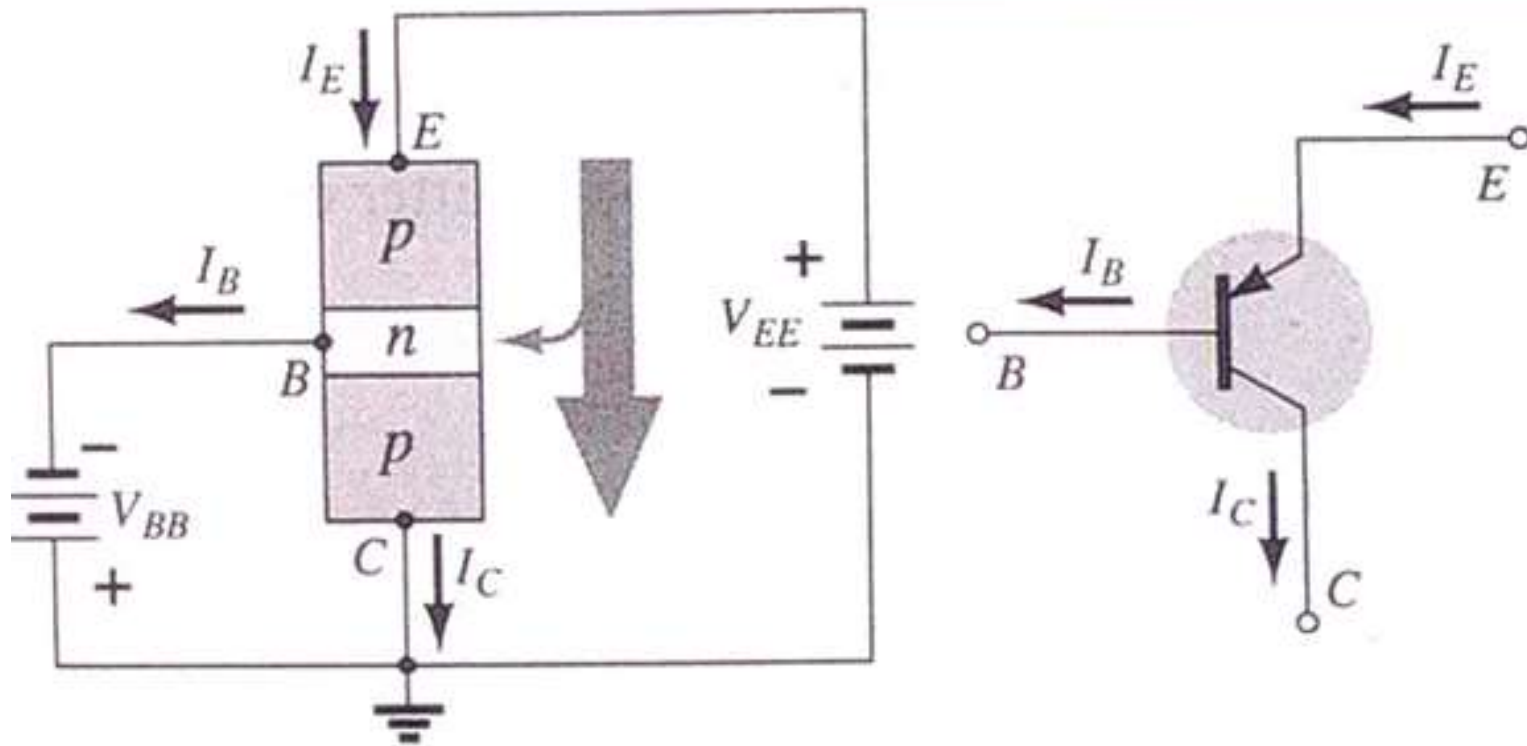
# Common-Collector Configuration of pnp Transistor




# Common Collector Input Characteristics

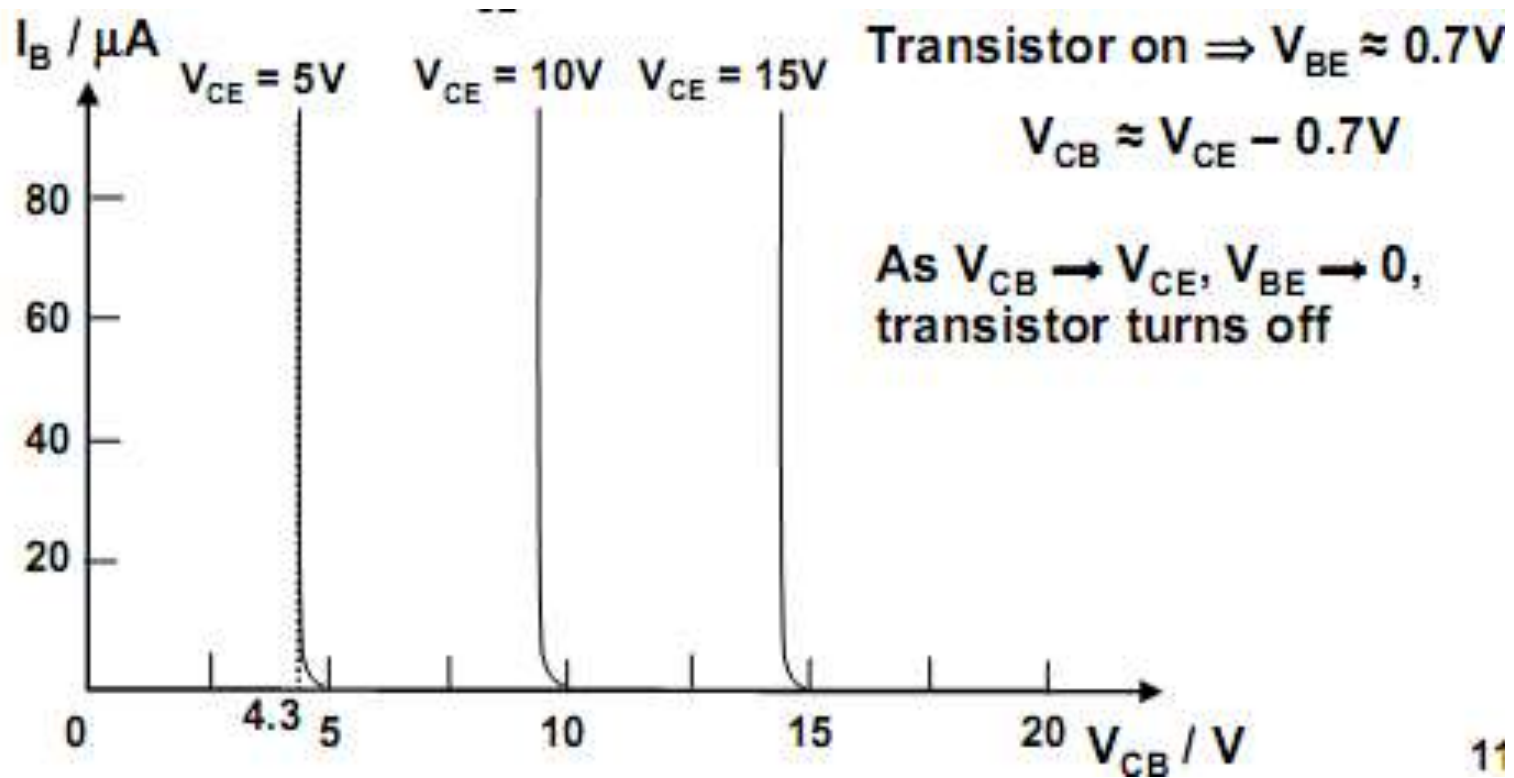

11


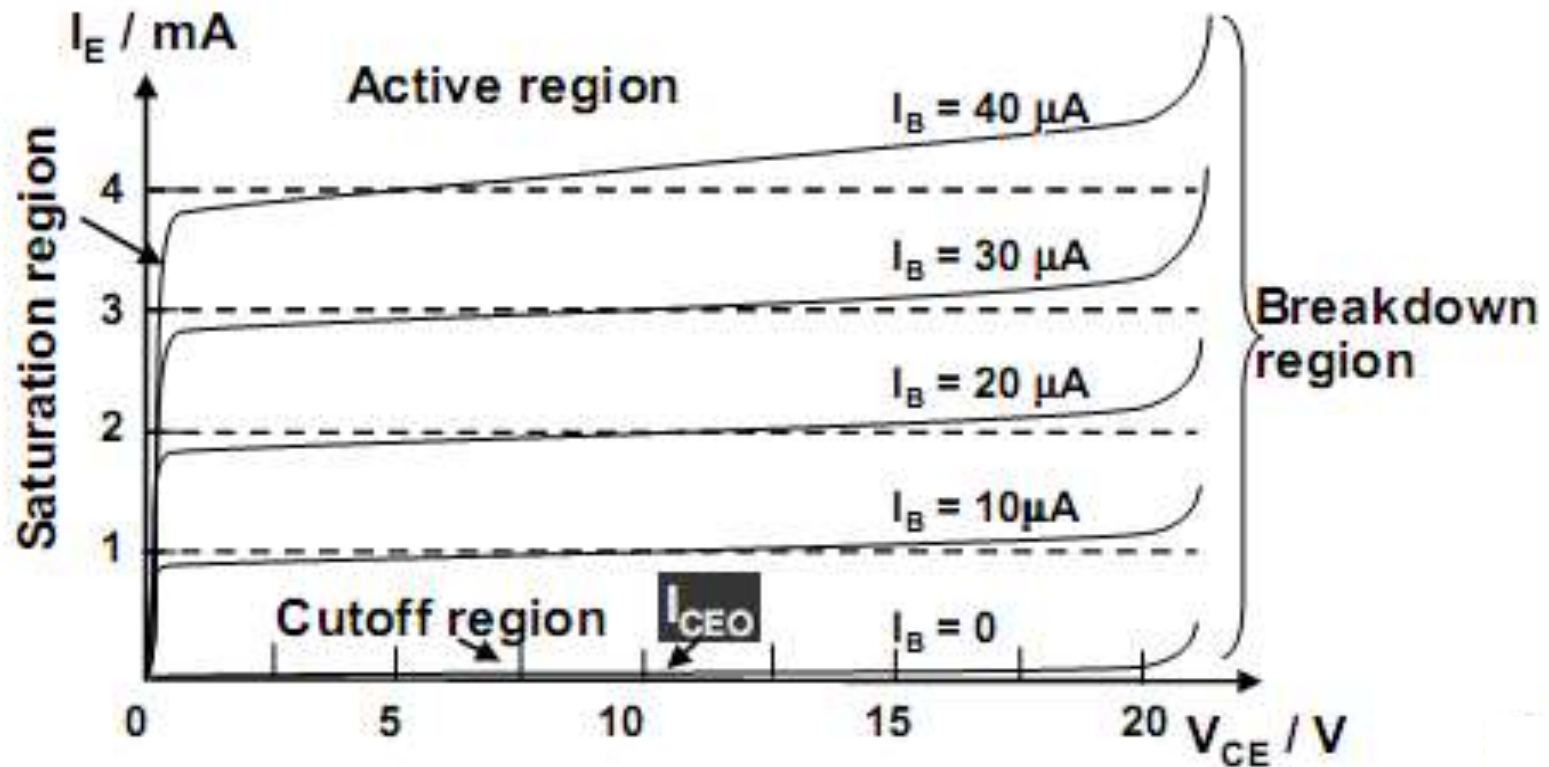
# Common Collector Output Characteristics



# Summary

- BJT consist of either a P-N-P or an N-P-N semiconductor structure.
- BJT has three leads called Emitter, Base, and Collector
- BJT has three configurations: common base, common emitter and common collector
- Transistor operates in 3 regions: Active, saturation and cut off



# Transistor Parameters

- At the end of this lecture, student will be able to :
  - Draw the equivalent circuit of a transistor
  - Explain about the transistor Parameters
  - Derive the relation between alpha, beta and gamma





# Topics

- Equivalent circuit of transistor
- Transistor Parameters
- Relation between  $\alpha$ ,  $\beta$  and  $\gamma$



# Transfer Characteristics Continued..

## Transfer characteristics

- It can be described by either the current gain or by the transconductance
- DC current gain  $h_{FE}$  or  $\beta$  is given by

$$\beta (h_{FE}) = I_C / I_B$$

- AC current gain  $h_{FE}$  is given by

$$h_{FE} = i_c / i_b$$

- Transconductance  $g_m$  is given approximately by

$$g_m \approx 40I_C \approx 40 I_E \text{ Siemens}$$



# Current Amplification Factors

$\beta$  = Common-emitter current gain

$\alpha$  = Common-base current gain

$\gamma$  = Common collector current gain

$$I_E = I_C + I_B$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

$$\alpha = \frac{\beta}{\beta + 1}$$



$$\beta = \frac{\alpha}{1 - \alpha}$$

$$\gamma = \beta + 1$$




# Common Base Transistor Circuit

Schematic  
symbols

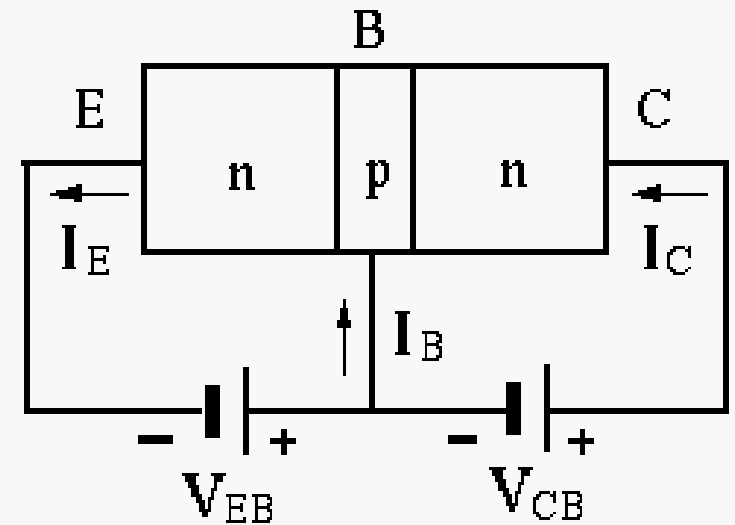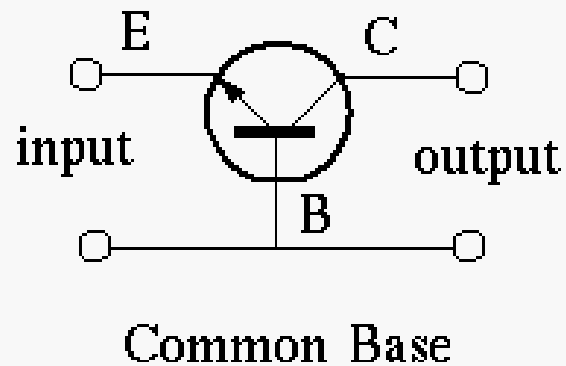

# Common Base Transistor Working


Dramatic  
symbol

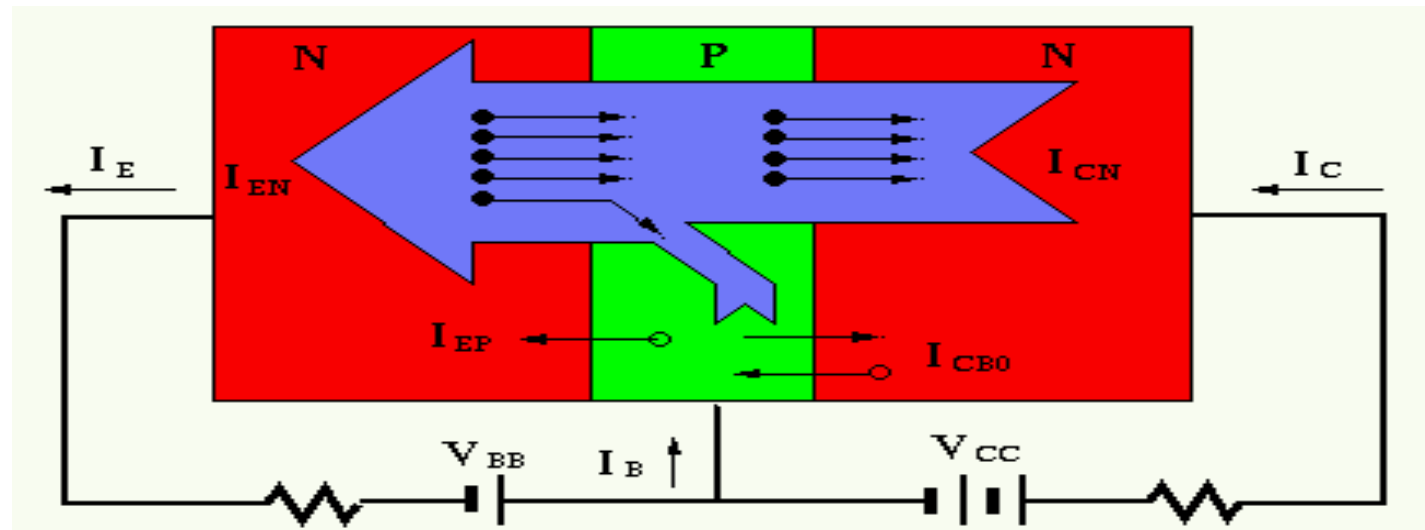

# Common Base DC current gain - PNP



Common Base - Active Bias mode:

$$I_C = \alpha_{DC} I_E + I_{CBO}$$

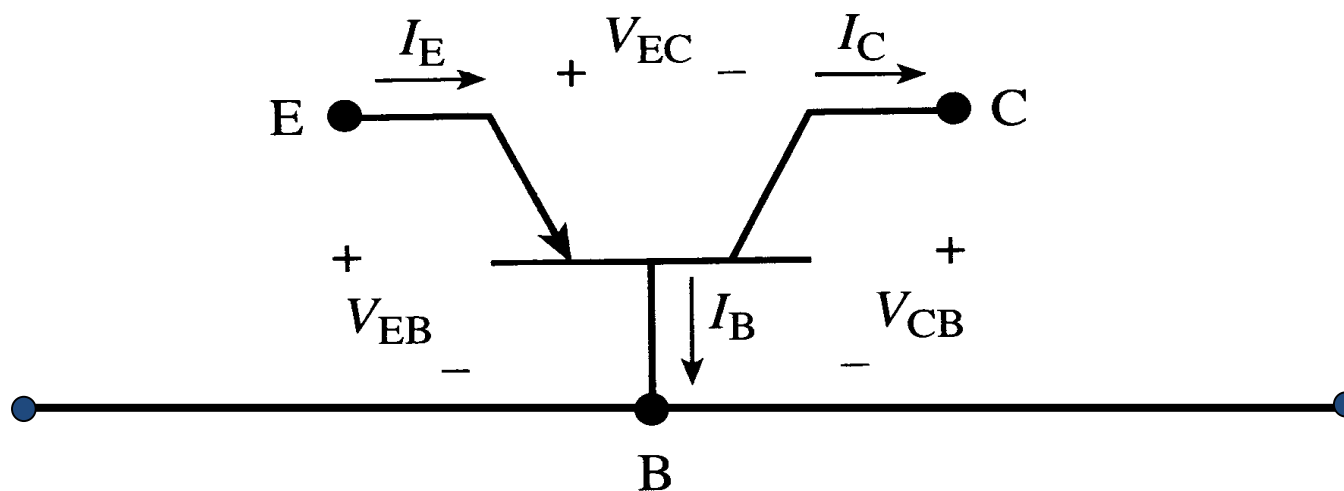

# Common Emitter Amplifier Circuit

Schematic  
symbols

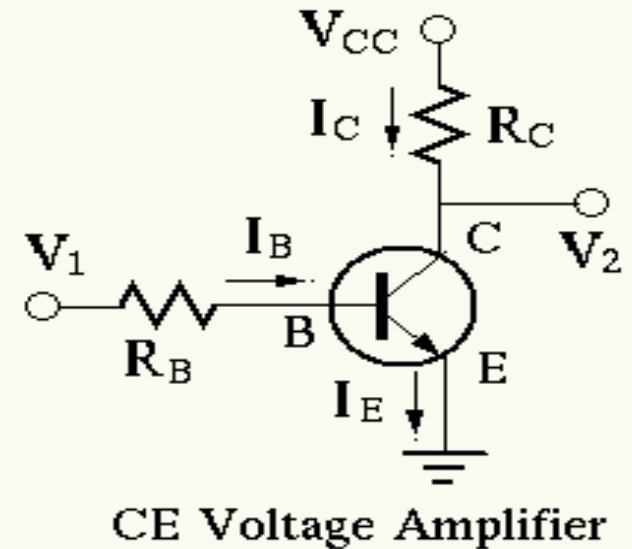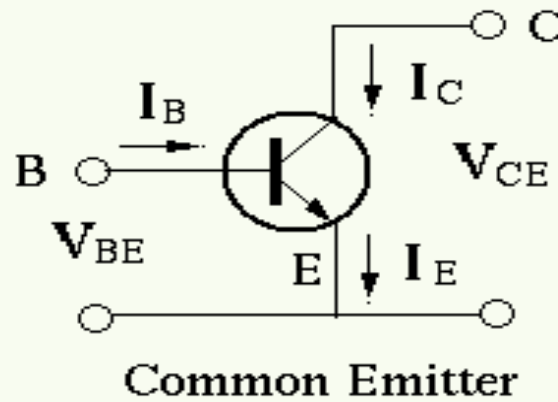

# Common Emitter Amplifier Equations

$$I_{C(max)} = \frac{V_{CC} - V_{CE(sat)}}{R_C} = I_{C(sat)}$$

$$I_{B(min)} = \frac{I_{C(sat)}}{\beta_{dc}}$$


$$\begin{aligned}\beta_{dc} &= \frac{\alpha_{dc}}{1 - \alpha_{dc}} \\ &= \frac{\frac{I_C - I_{CO}}{I_E}}{1 - \frac{I_C - I_{CO}}{I_E}} = \frac{I_C - I_{CO}}{I_E - I_C + I_{CO}} \\ &= \frac{I_C - I_{CO}}{I_B + I_{CO}}\end{aligned}$$





# Common Emitter Amplifier Working

Dramatic  
symbol

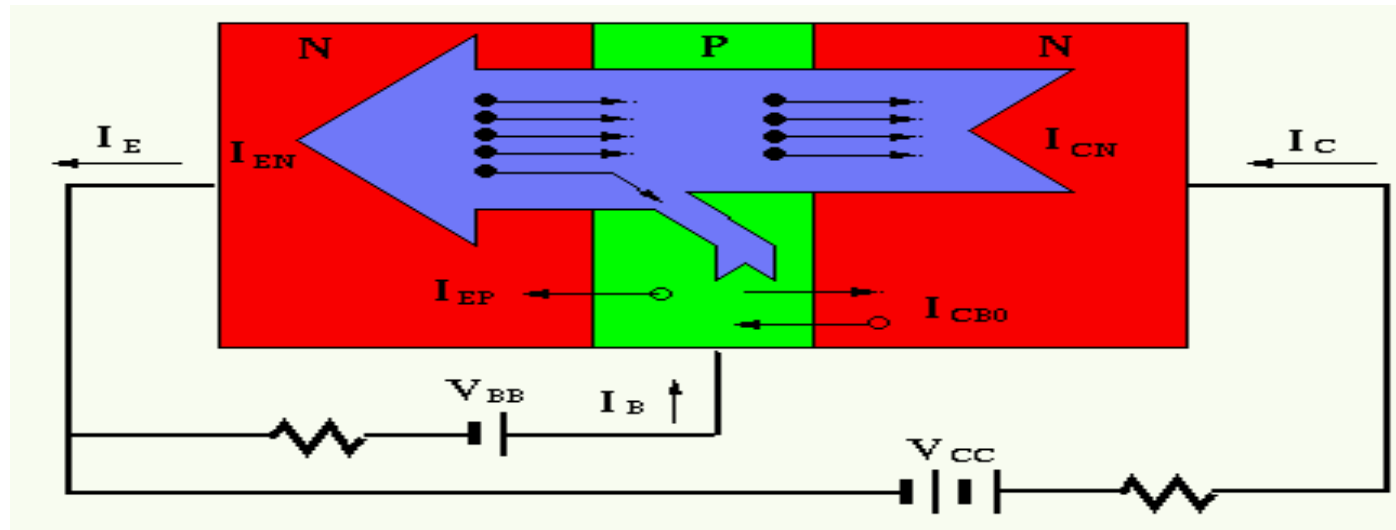

# Common Emitter DC current gain - PNP

Common Emitter Active Bias mode:

$$I_E = \beta_{DC} I_B + I_{CEO}$$

$$I_C = \alpha_{DC} I_E + I_{CBO}$$

$$= \alpha_{DC} (I_C + I_B) + I_{CBO}$$

$$\beta_{DC} = \alpha_{DC} / (1 - \alpha_{DC})$$

GAIN !!


$$I_C = \frac{\alpha_{DC} I_B + I_{CBO}}{1 - \alpha_{DC}}$$

$$\alpha_{DC} = \beta_{DC} / (1 + \beta_{DC})$$

$$I_{CEO} = I_{CBO} / (1 - \alpha_{DC})$$



# Common Collector Amplifier

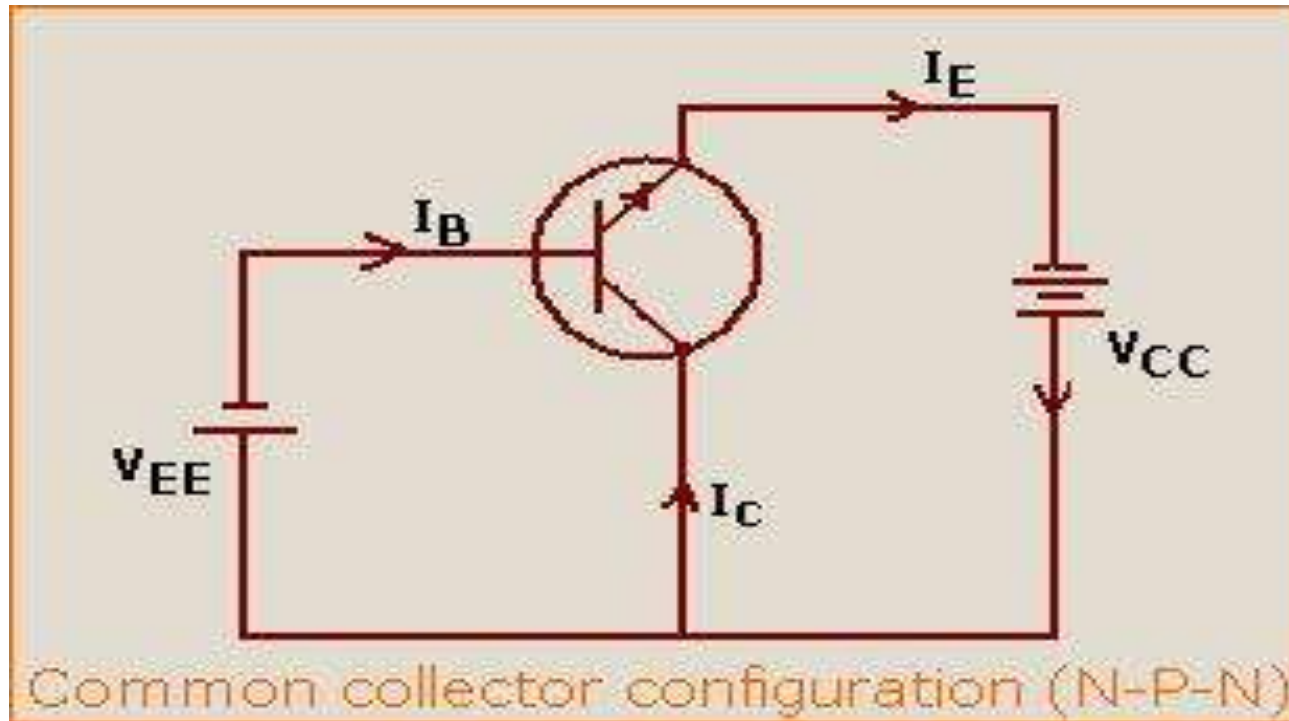

# Common Collector Features

- Common Collector is also called emitter-follower (EF).
- It is called common-collector configuration since both the signal source and the load share the collector terminal as a common connection point.
- Output voltage is obtained at emitter terminal.
- Input characteristic of common-collector configuration is similar with common-emitter configuration.
- Common-collector circuit configuration is provided with the load resistor connected from emitter to ground.
- It is used primarily for **impedance-matching** purpose since it has high input impedance and low output impedance.






# Characteristics of Different Transistor Configurations

Characteristic	Common Base	Common Emitter	Common Collector
Input Impedance	Low	Medium	High
Output Impedance	Very High	High	Low
Phase Angle	0°	180°	0°
Voltage Gain	High	Medium	Low
Current Gain	Low	Medium	High
Power Gain	Low	Very High	Medium



# Comparison of Different Configuration

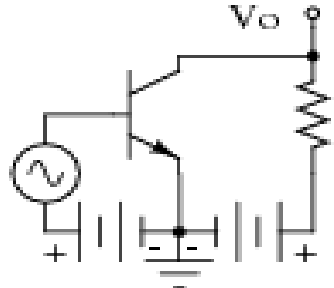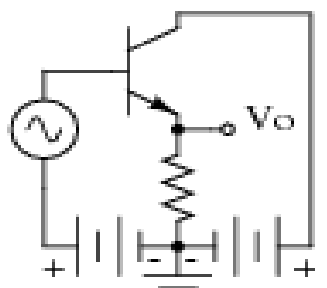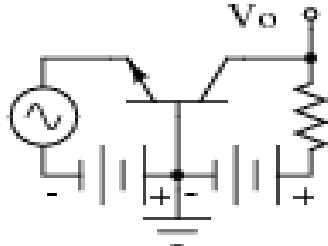Basic circuit	Common emitter	Common collector	Common base
			
Voltage gain	high	less than unity	high, same as CE
Current gain	high	high	less than unity
Power gain	high	moderate	moderate
Phase inversion	yes	no	no
Input impedance	moderate $\approx 1\text{ k}$	highest $\approx 300\text{ k}$	low $\approx 50\ \Omega$
Output impedance	moderate $\approx 50\text{ k}$	low $\approx 300\ \Omega$	highest $\approx 1\text{ Meg}$

# Problems

- **Example 2.1**

A certain npn transistor has a base current of  $80\mu\text{A}$  and a collector current of  $2\text{mA}$ . Calculate  $\alpha$ ,  $\beta$  and  $I_E$   
( $\alpha=.96$ ,  $\beta=25$ ,  $I_E=2.08\text{mA}$ )

- **Example 2.2**

For a transistor  $\alpha=.98$ ,  $I_B=50\mu\text{A}$ . Find values of  $I_C$ ,  $I_E$  and  $\beta$



# Summary

- Behavior can be described by the current gain,  $h_{FE}$  or by the transconductance,  $g_m$  of the device
- CE configuration will provide the current gain .
- Voltage gain is provided by CB configuration.





# Junction Field Effect Transistor

- At the end of this lecture, student will be able to :
  - Define JFET
  - Explain the construction of JFET
  - Explain the operation of JFET
  - Classify JFET and BJT




# Topics


- JFET basics
- JFET construction
- JFET operation
- JFET characteristics



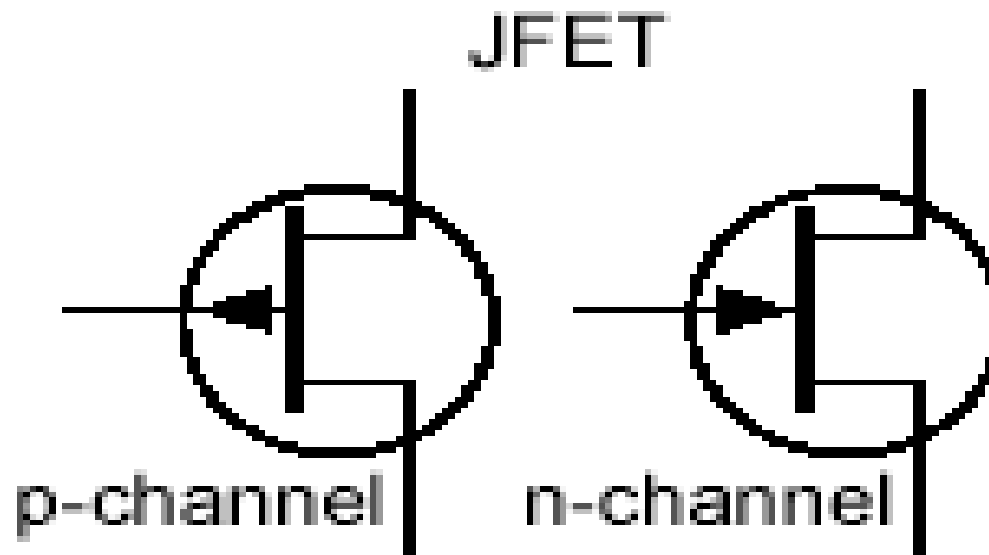
# JFET (Junction Field Effect Transistor)



# JFET continued..

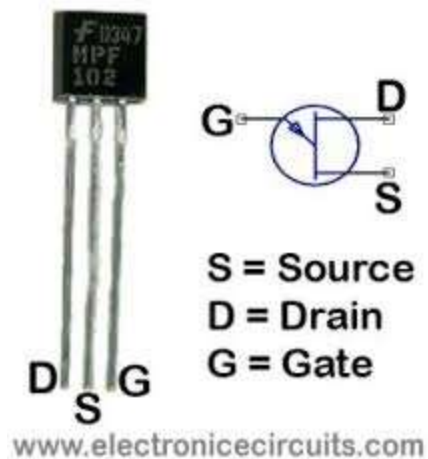

# JFET Construction

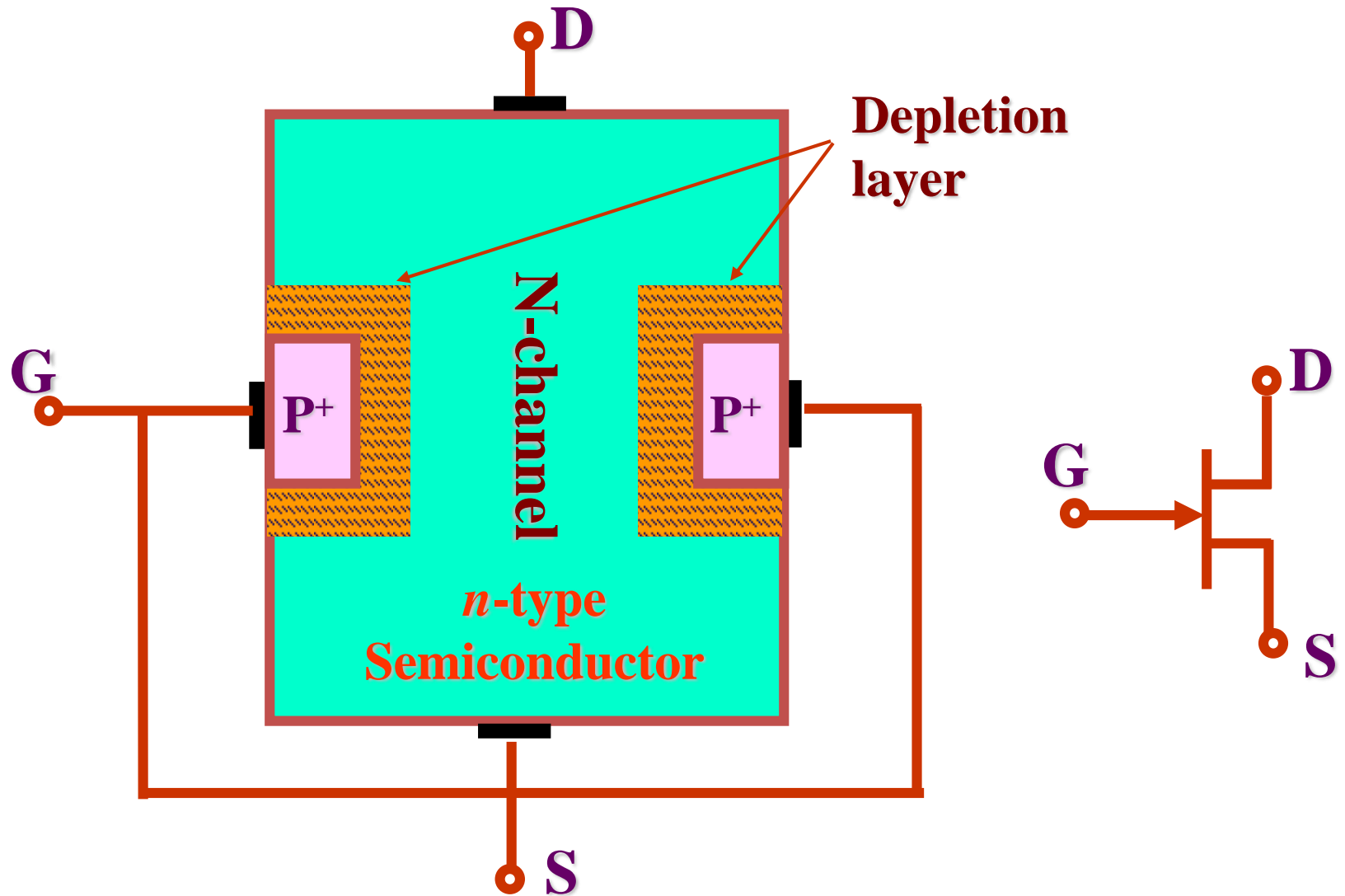


# JFET Construction Continued..


- An n- channel is formed between two p-type layers which are connected to the gate.
- Majority carrier electrons flow from the source and exit the drain, forming the drain current.
- The pn junction is reverse biased during normal operation, and this widens the depletion layers which extend into the n channel only (since the doping of the p regions is much larger than that of the n channel). As the depletion layers widen, the channel narrows, restricting current flow.



# $n$ - Channel and $p$ -Channel JFET

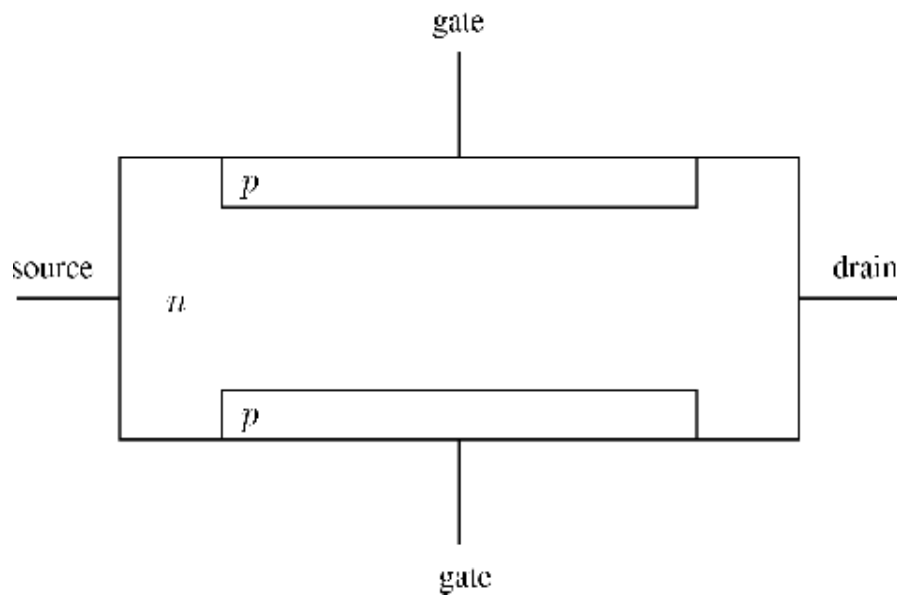


$n$ - channel JFET

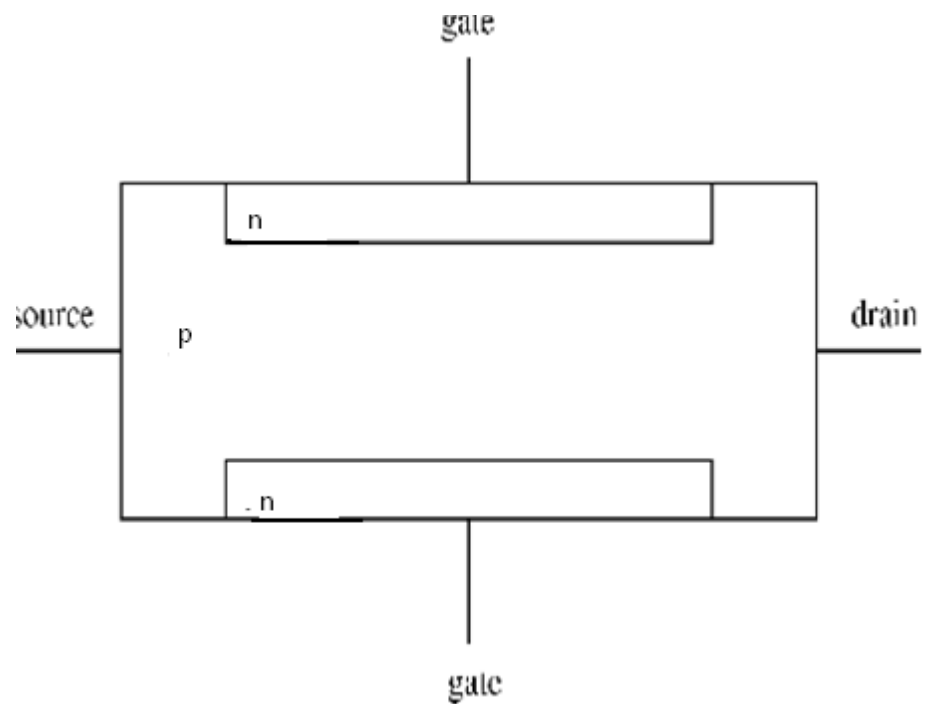

$p$ - channel JFET




# JFET operation under $v_{DS}=0$

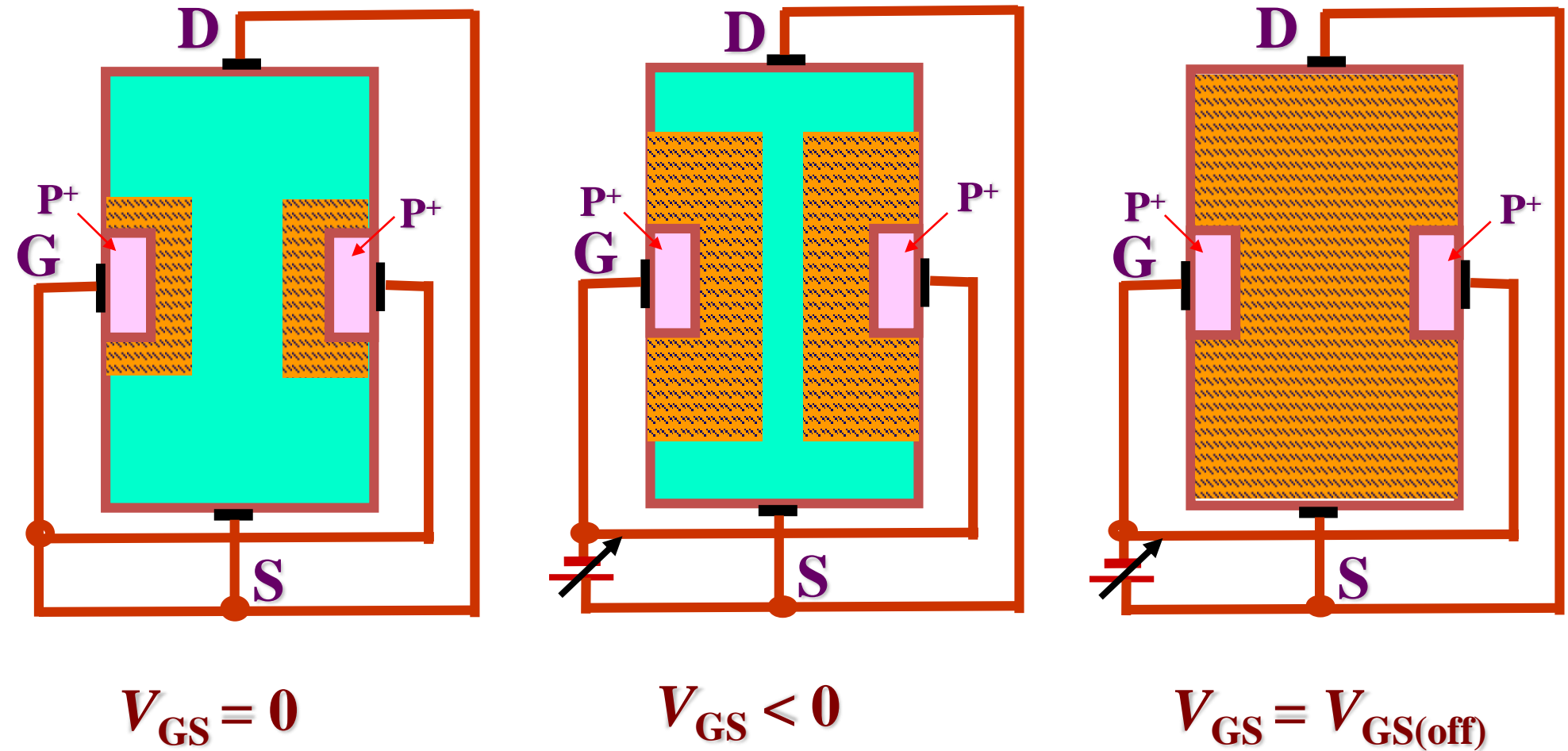



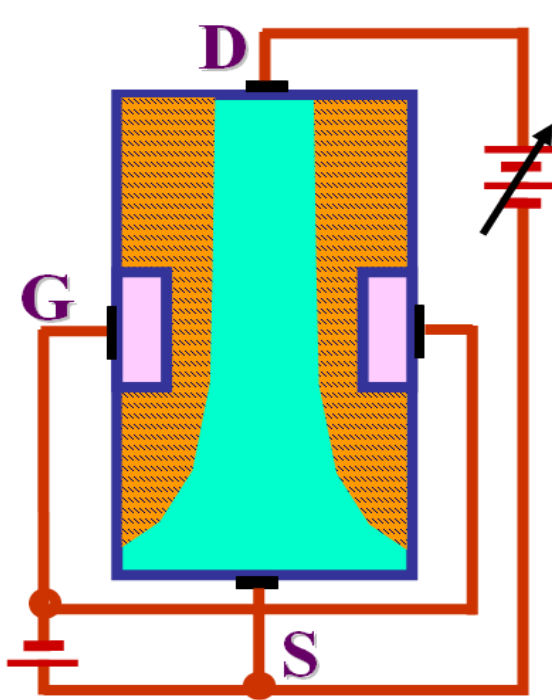
## Effect of $V_{DS}$ on $I_D$ for $V_{GS(off)} < V_{GS} < 0$




$$V_{GD} > V_{GS}$$

Triode region

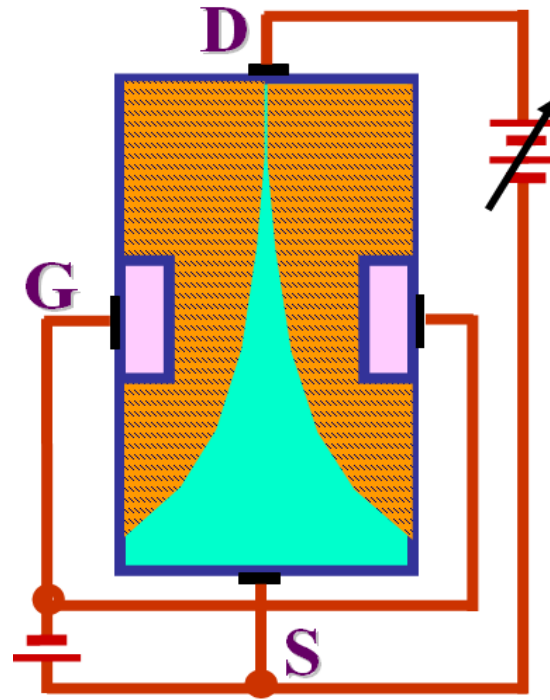

$$V_{GD} = V_{GS(off)}$$


Pinch off

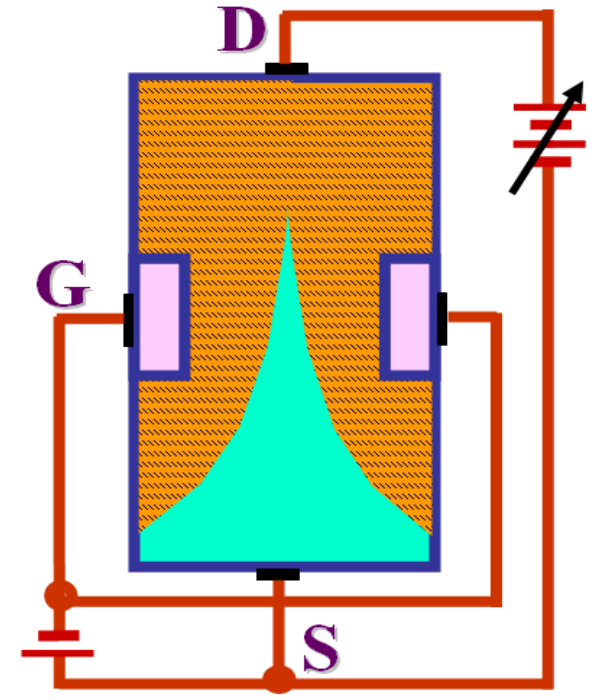

$$V_{GD} < V_{GS(off)}$$


Saturation region

# N-JFET Characteristics

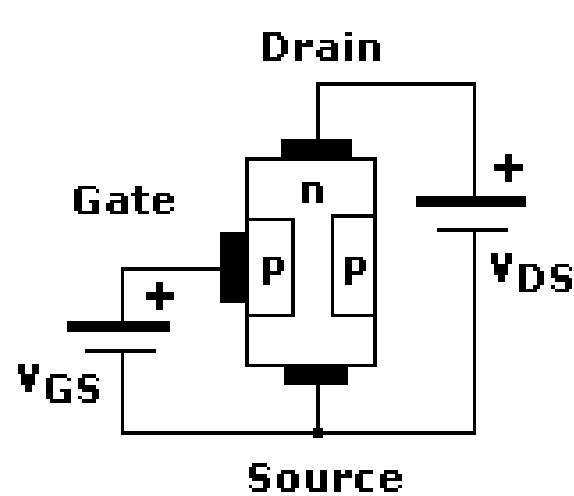


NJFET  
Characteristics

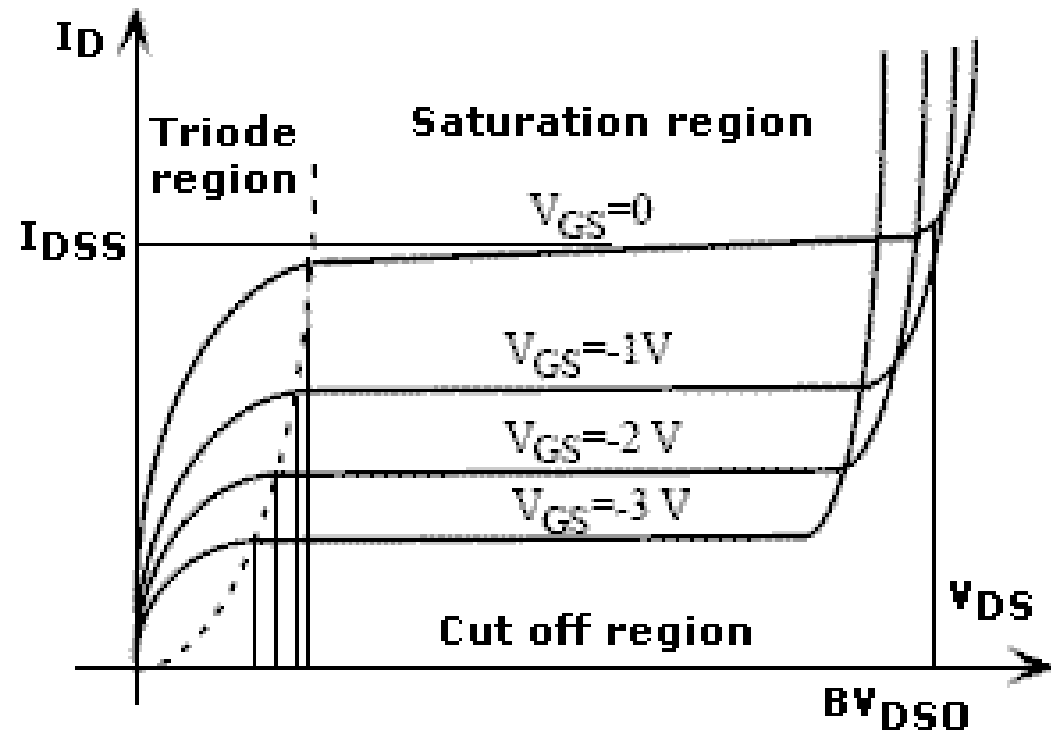
[www.electronicsarea.com](http://www.electronicsarea.com)




# Operation of JFET: Ohmic Region

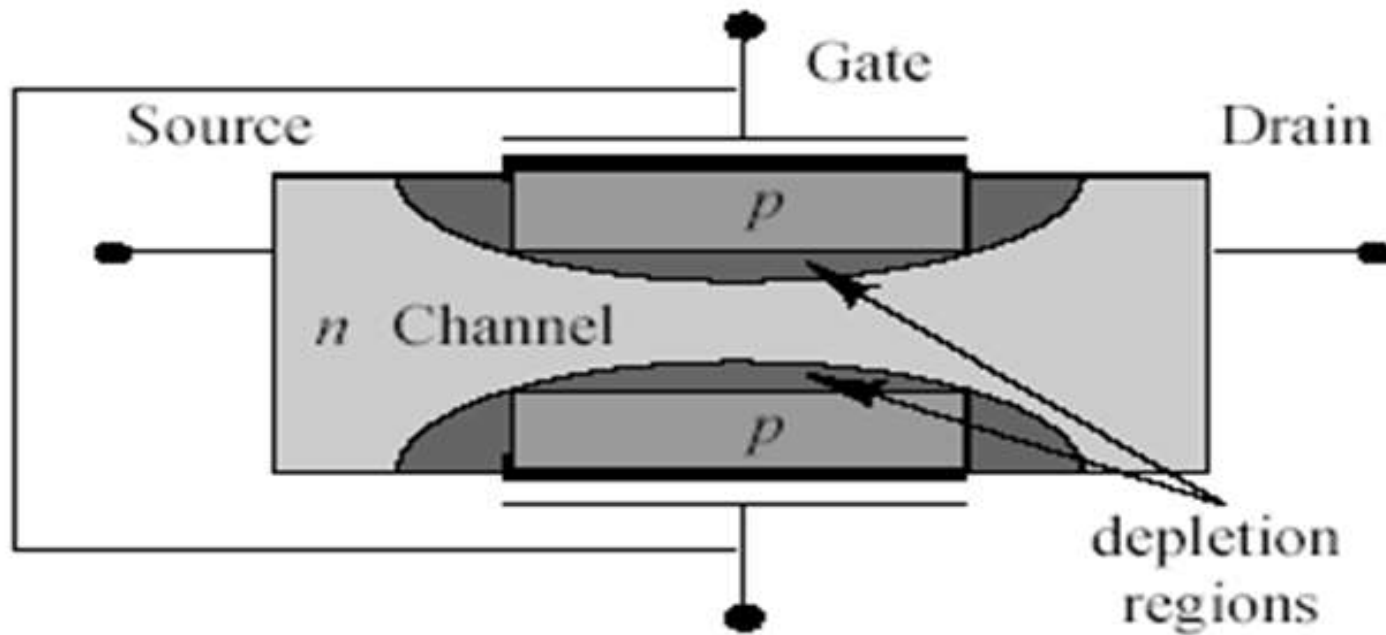


# Operation of JFET: Saturation Region

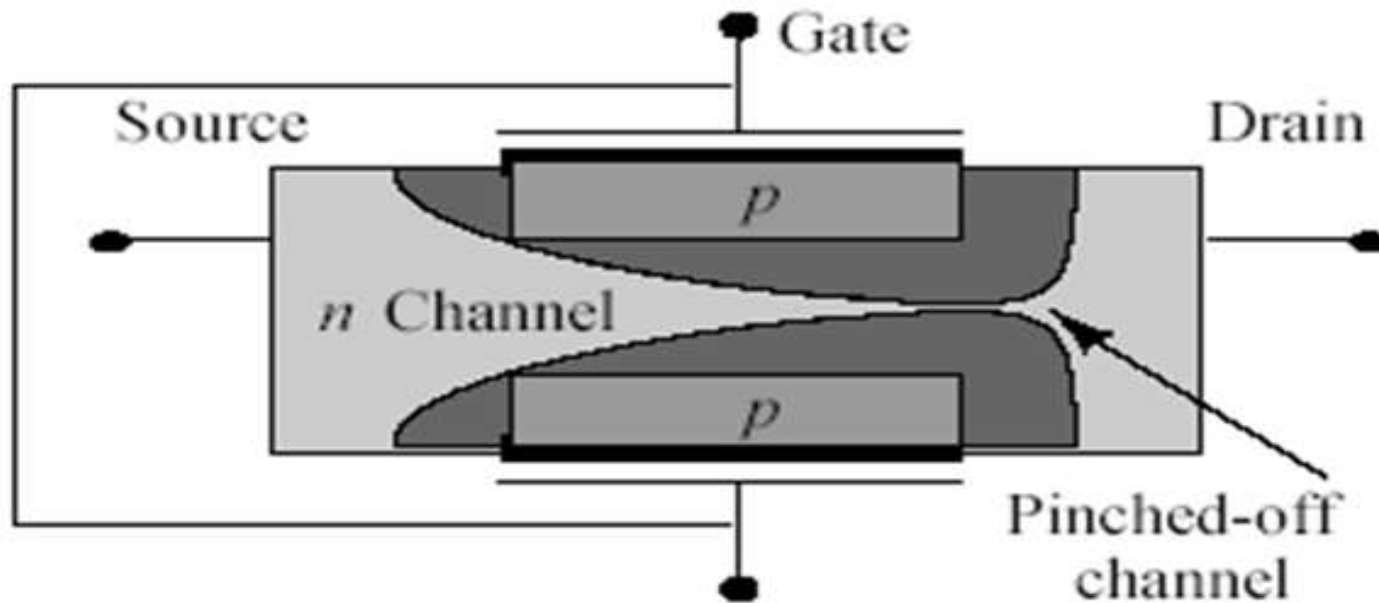


# Operation of JFET: Breakdown Region

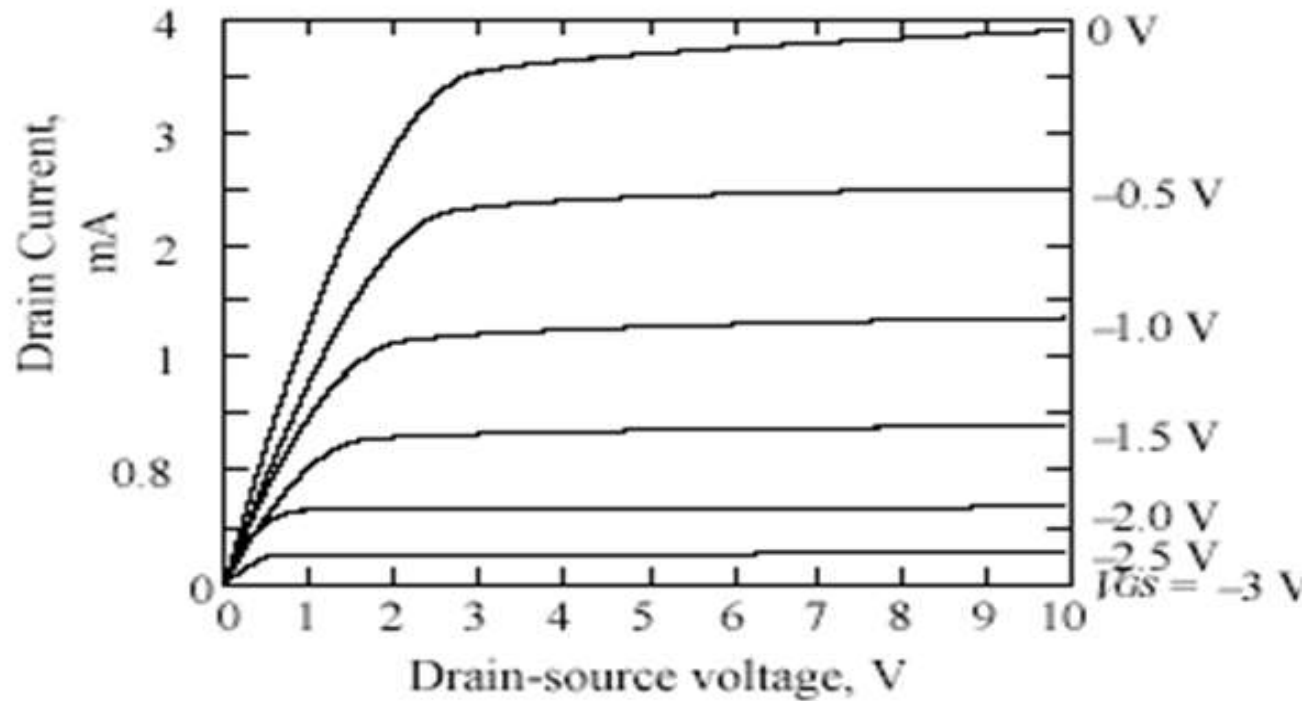

# Characteristic Curve of N Channel JFET

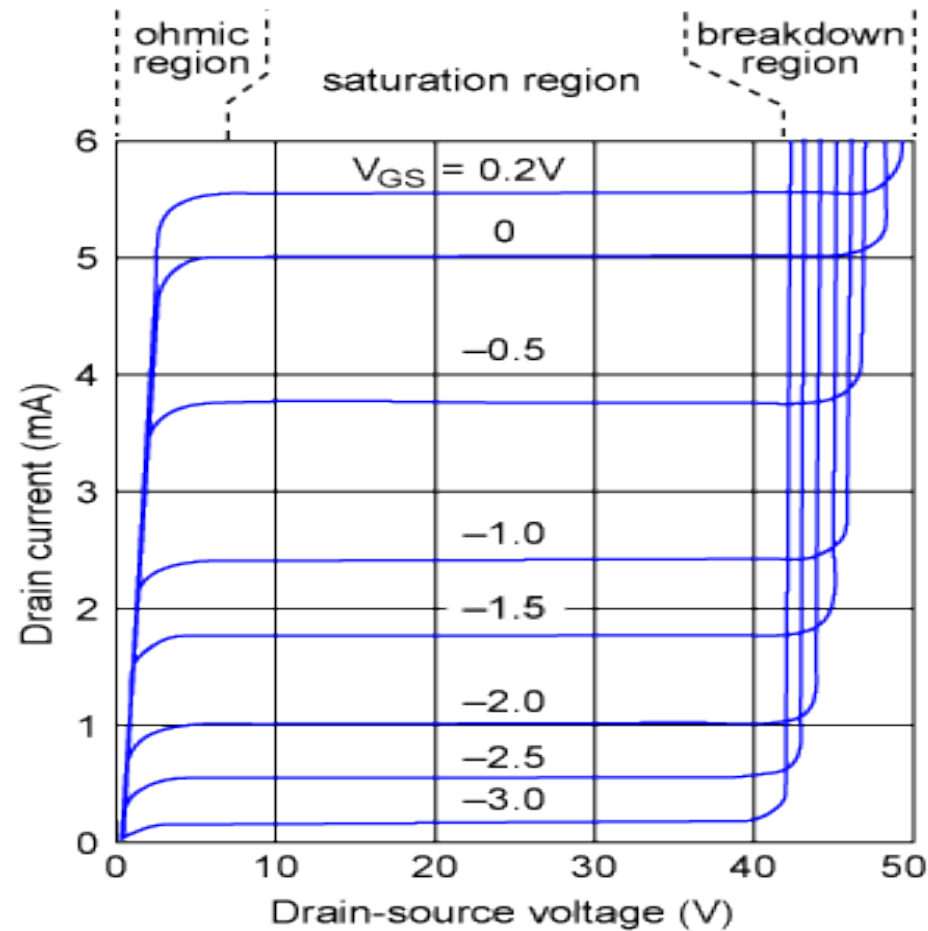

# JFET Working

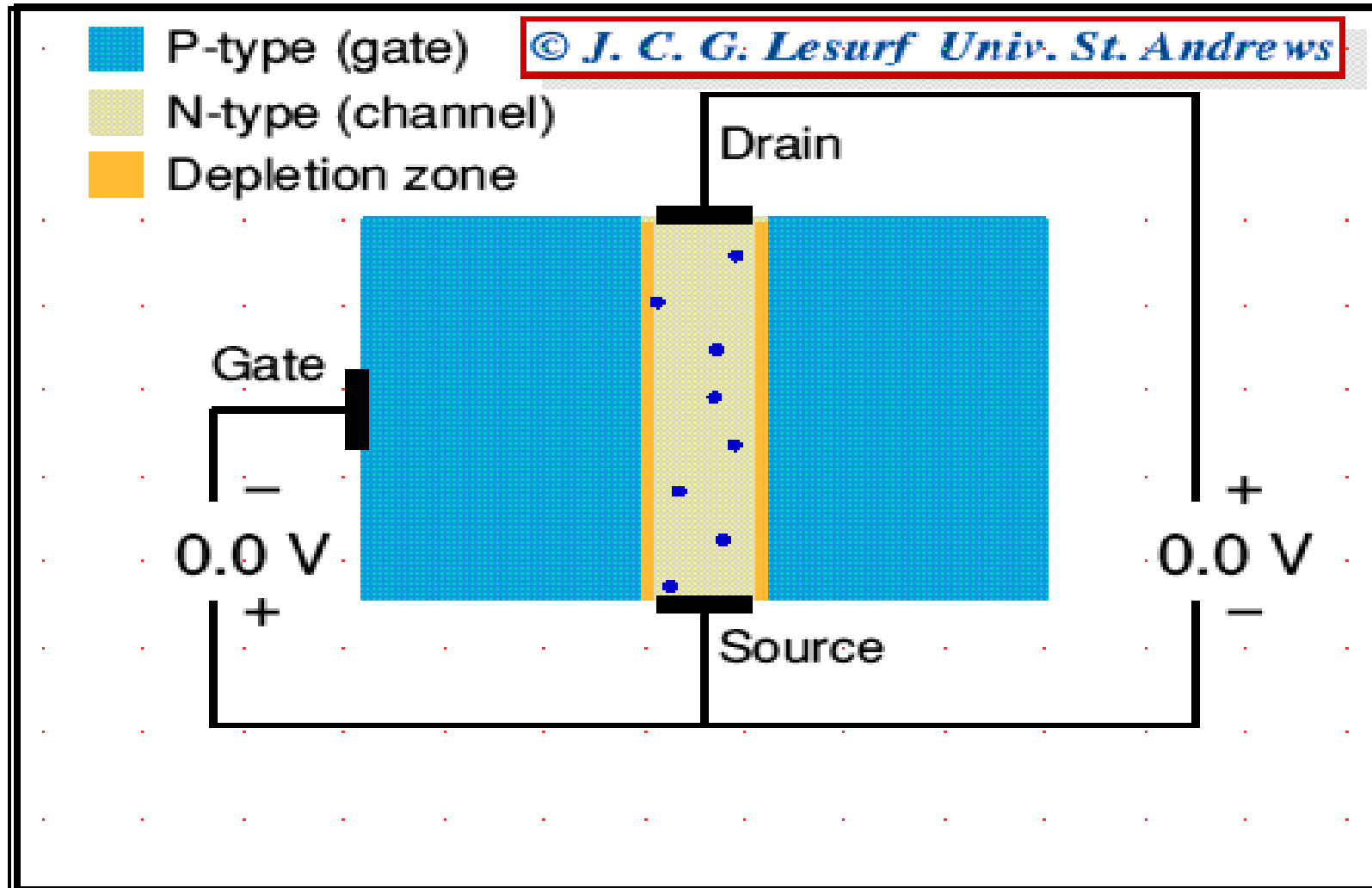

# JFET Operation





# JFET Equations

- The following equations describe the operation of n-channel JFETs (and of depletion-mode MOSFETs; those for enhancement-mode MOSFETs are slightly different). They also apply to p-channel JFETs by substituting  $v_{SG}$  for  $v_{GS}$  and  $v_{SD}$  for  $v_{DS}$ .

Cut – off region :  $v_{GS} < -V_P$

Ohmic region :  $v_{DS} < 0.25(v_{GS} + V_P)$ ,  $v_{GS} > -V_P$

$$R_{DS} = \frac{V_P^2}{2I_{DSS}(v_{GS} + V_P)} \quad (\text{equivalent drain - to - source resistance})$$

$$i_D \approx \frac{v_{DS}}{R_{DS}}$$

Saturation region :  $v_{DS} \geq v_{GS} + V_P$ ,  $v_{GS} > -V_P$


$$i_D = \frac{I_{DSS}}{V_P^2} (v_{GS} + V_P)^2$$

Breakdown region :  $v_{DS} > V_B$


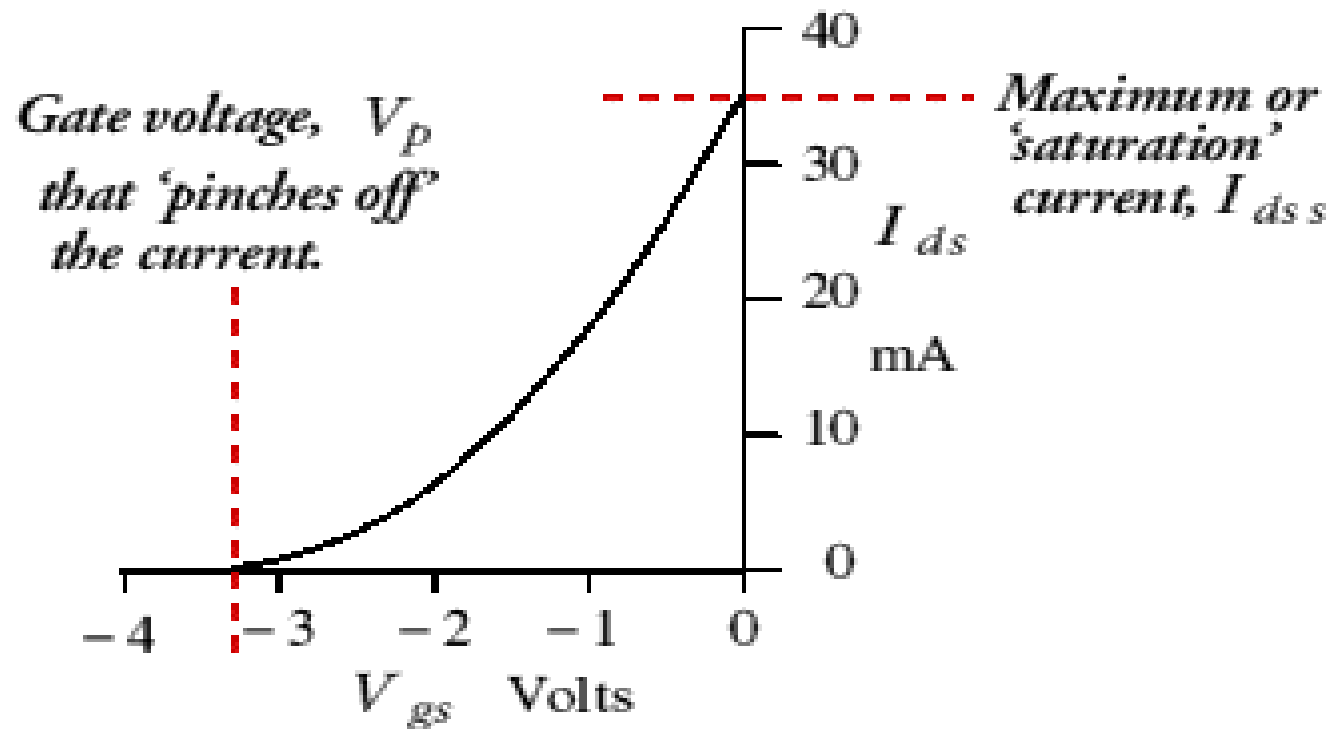
# JFET Transfer characteristic

Simplified characteristic curve for any drain-source voltage above a few volts.



# JFET Transfer characteristic continued..

Hence a large increase in drain-source:

- ‘pulls harder’, trying to drag the electrons more quickly from source to drain.
- ‘squeezes down’ the channel making it harder for the electrons to get through.
- These effects tend to cancel out, leaving the current the same at all high drain-source voltage.



# Summary

- JFETS are unipolar devices.
- Gate, Drain and Source are the terminals of JFET
- JFET is a voltage controlled device.
- JFET can work in 3 regions which are Ohmic, saturation and cut off.

