

# Basic Laws of Electric Circuits

## Nodal Analysis



## Nodal analysis

Analysis using KCL to solve for voltages at each common node of the network

### Nodal analysis procedure:


1. Determine the number of common nodes and reference node within the network.
2. Apply KCL at each of the common nodes in the network
3. Solve the resulting simultaneous linear equation for the nodal voltages.



# Circuit Analysis

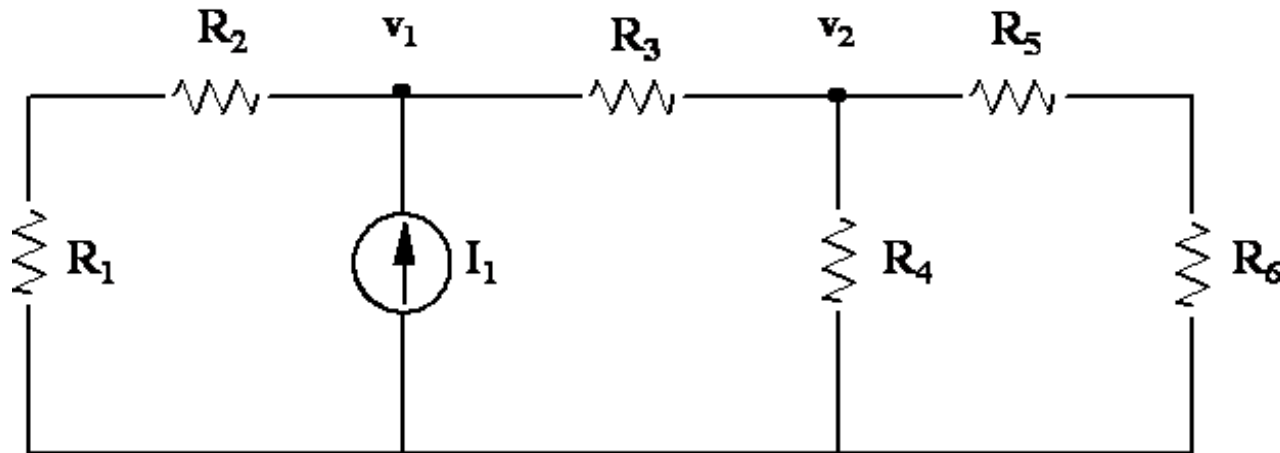
## Nodal Analysis:

Given the following circuit. Set-up the equations to solve for  $V_1$  and  $V_2$ .



# Circuit Analysis

## Nodal Analysis: Nodal equations.

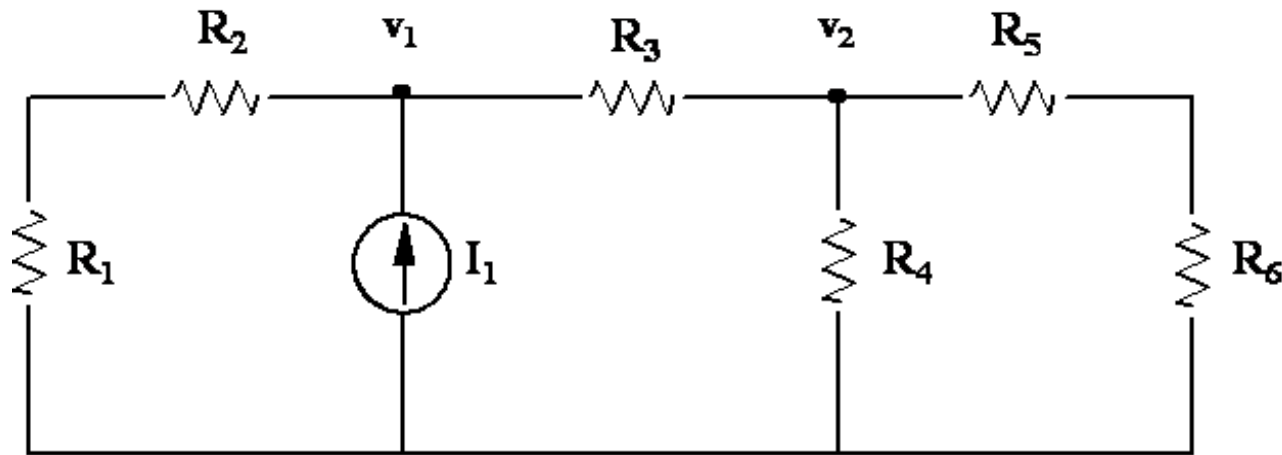

$$\frac{V_1}{R_1 + R_2} + \frac{V_1 - V_2}{R_3} = I_1 \quad \text{Eq 1}$$

$$\frac{V_2 - V_1}{R_3} + \frac{V_2}{R_4} + \frac{V_2}{R_5 + R_6} = 0 \quad \text{Eq 2}$$



# Circuit Analysis

Nodal Analysis: Set up for solution.

$$\frac{V_1}{R_1 + R_2} + \frac{V_1 - V_2}{R_3} = I_1 \quad \text{Eq 1}$$

$$\frac{V_2 - V_1}{R_3} + \frac{V_2}{R_4} + \frac{V_2}{R_5 + R_6} = 0 \quad \text{Eq 2}$$

---


$$\left( \frac{1}{R_1 + R_2} + \frac{1}{R_3} \right) V_1 - \left( \frac{1}{R_3} \right) V_2 = I_1 \quad \text{Eq 3}$$

$$-\left( \frac{1}{R_3} \right) V_1 + \left( \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5 + R_6} \right) V_2 = 0 \quad \text{Eq 4}$$



# Circuit Analysis


## Nodal Analysis:

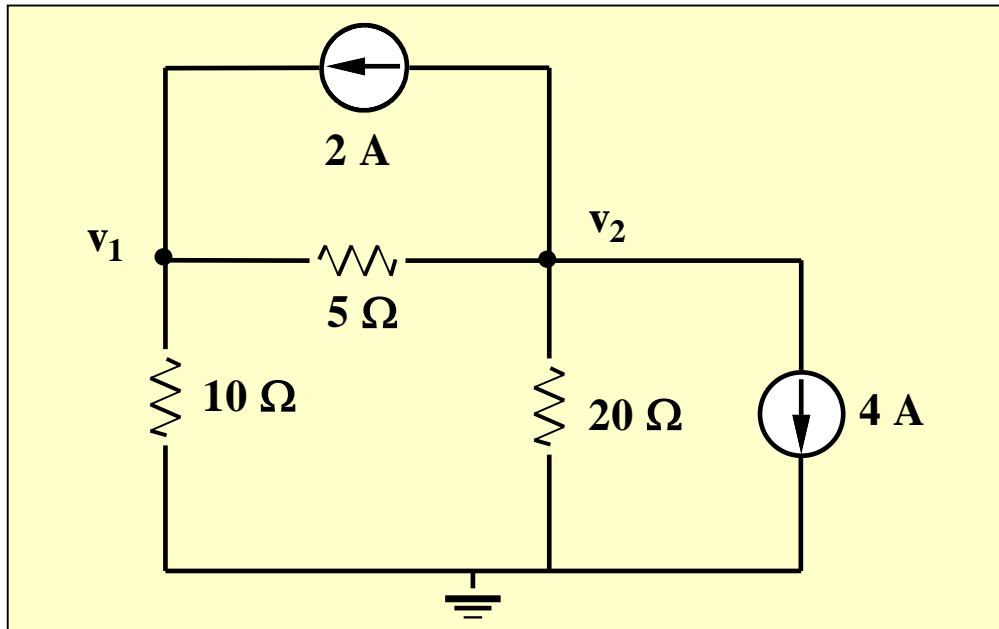

For the given circuit  
Find  $V_1$  and  $V_2$ .

# Circuit Analysis

## Nodal Analysis:

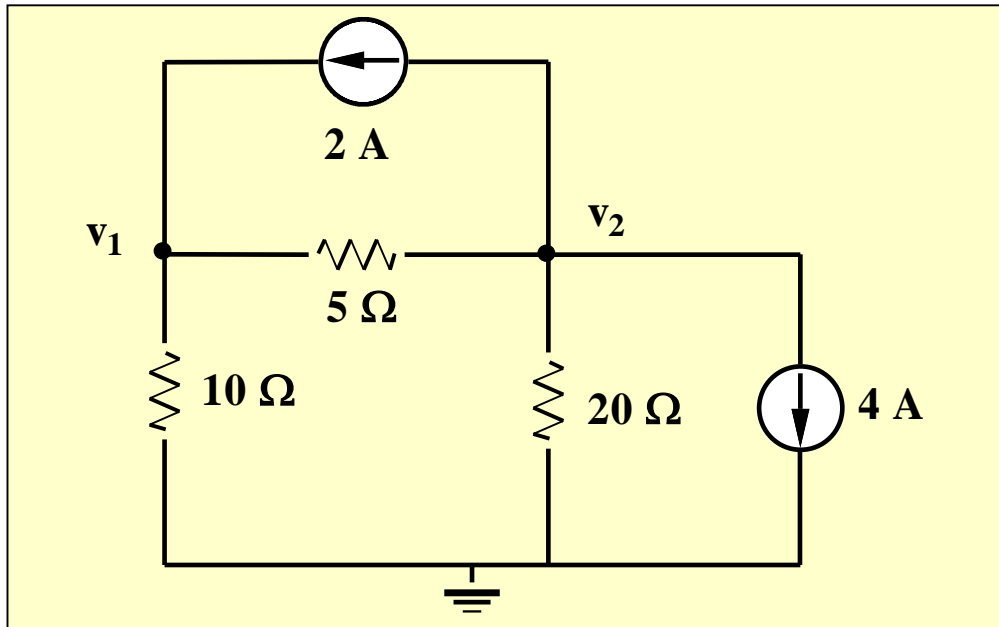

At  $v_1$ :

$$\frac{V_1}{10} + \frac{V_1 - V_2}{5} = 2$$

Eq 1

At  $v_2$ :

$$\frac{V_2 - V_1}{5} + \frac{V_2}{20} = -6$$

Eq 2



# Circuit Analysis

## Nodal Analysis: Clearing Equations;

From Eq 1:

$$V_1 + 2V_1 - 2V_2 = 20$$

or

$$3V_1 - 2V_2 = 20$$

Eq 3

From Eq 2:

$$4V_2 - 4V_1 + V_2 = -120$$

or

$$-4V_1 + 5V_2 = -120$$

Eq 4


$$\text{Solution: } V_1 = -20 \text{ V, } V_2 = -40 \text{ V}$$





# Circuit Analysis

## Nodal Analysis: With voltage source.

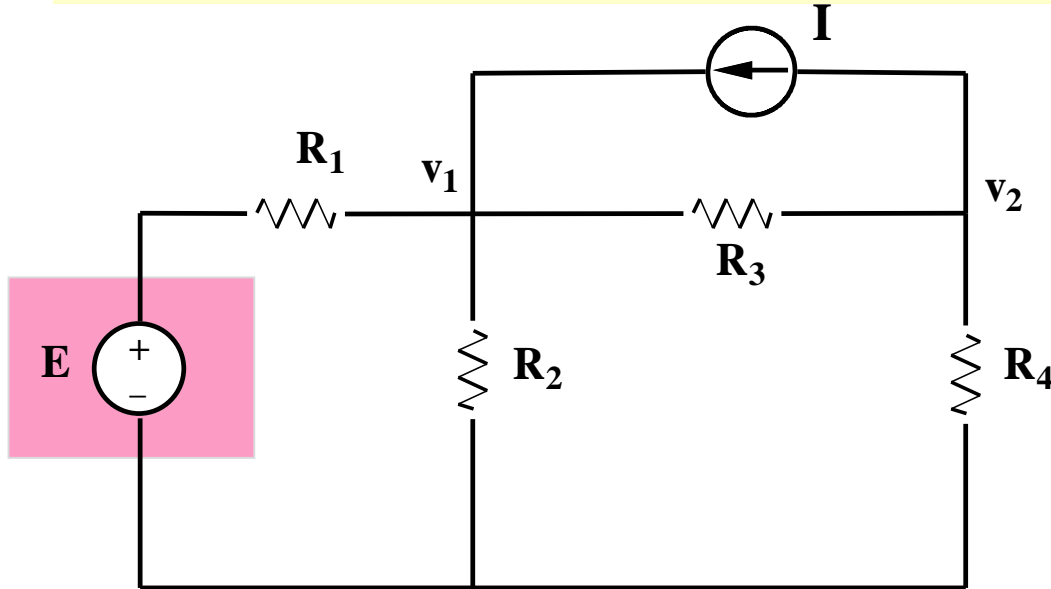

At  $V_1$ :

$$\frac{V_1 - E}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_3} = I \quad \text{Eq 1}$$


At  $V_2$ :

$$\frac{V_2}{R_4} + \frac{V_2 - V_1}{R_3} = -I \quad \text{Eq 2}$$



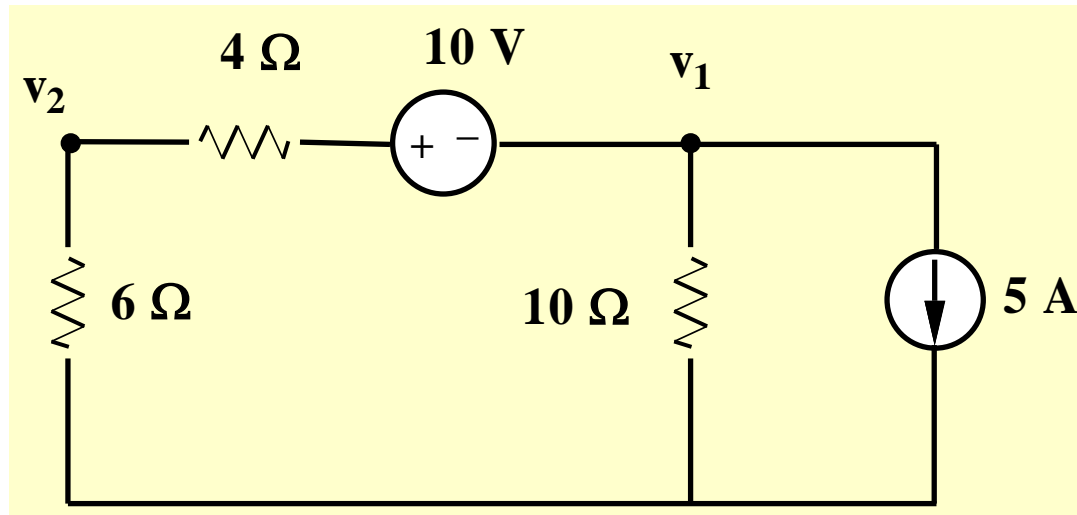
# Circuit Analysis

Nodal Analysis: Numerical example with voltage source.



# Circuit Analysis

## Nodal Analysis: Continued...

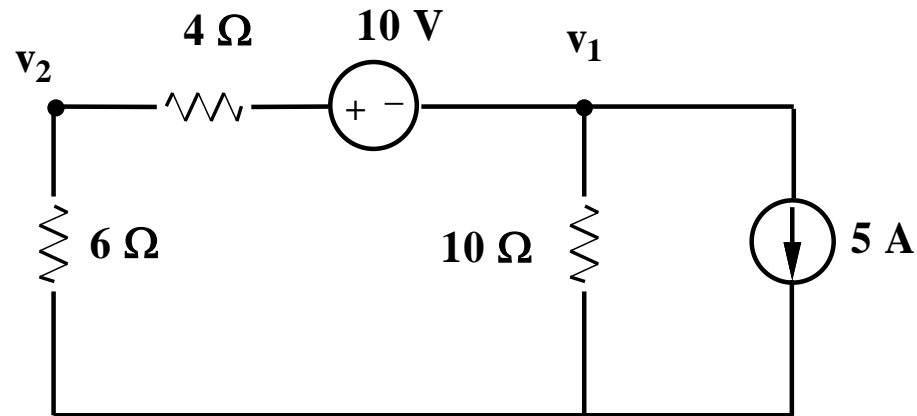

At  $v_1$ :

$$\frac{V_1}{10} + \frac{V_1 + 10 - V_2}{4} = -5 \quad \text{Eq 1}$$

At  $v_2$ :

$$\frac{V_2}{6} + \frac{V_2 - 10 - V_1}{4} = 0 \quad \text{Eq 2}$$



# Circuit Analysis

## Nodal Analysis: Continued

Clearing Eq 6.15

$$4V_1 + 10V_1 + 100 - 10V_2 = -200$$

or

$$14V_1 - 10V_2 = -300$$

Eq 3

Clearing Eq 6.16

$$4V_2 + 6V_2 - 60 - 6V_1 = 0$$

or

$$-6V_1 + 10V_2 = 60$$

Eq 4


$$V_1 = -30 \text{ V}, V_2 = -12 \text{ V}$$




# Circuit Analysis
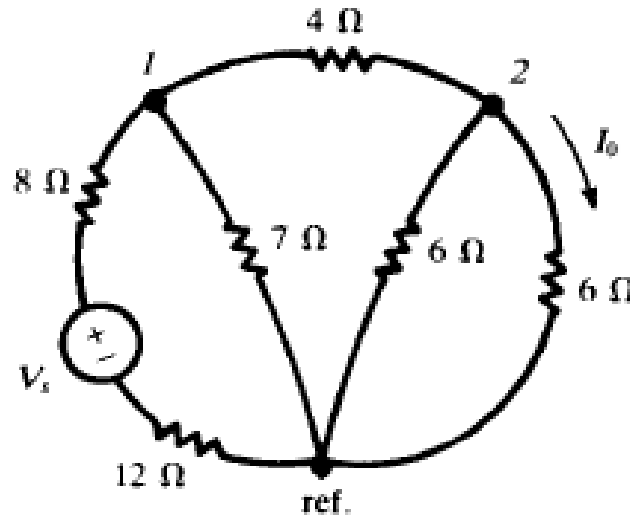
## Problem

For the network shown in Fig, find  $V_s$  which makes  $I_o = 7.5 \text{ mA}$ .



Solution:

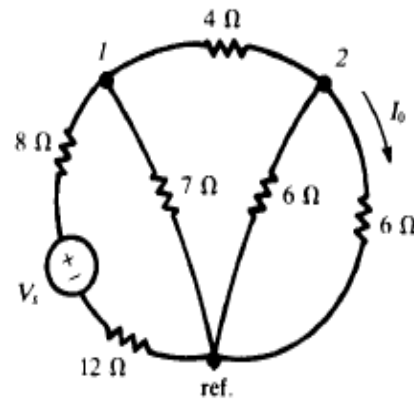

$$\begin{bmatrix} \frac{1}{20} + \frac{1}{7} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{4} + \frac{1}{6} + \frac{1}{6} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_s/20 \\ 0 \end{bmatrix}$$

Solving for  $V_2$ ,

$$V_2 = \frac{\begin{vmatrix} 0.443 & V_s/20 \\ -0.250 & 0 \end{vmatrix}}{\begin{vmatrix} 0.443 & -0.250 \\ -0.250 & 0.583 \end{vmatrix}} = 0.0638V_s$$

Then

$$7.5 \times 10^{-3} = I_0 = \frac{V_2}{6} = \frac{0.0638V_s}{6}$$


from which  $V_s = 0.705 \text{ V}$ .




# Circuit Analysis
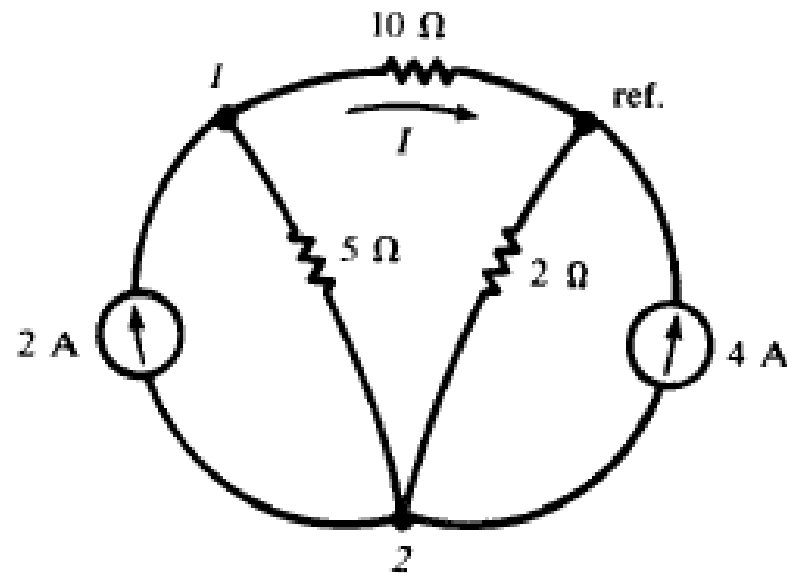
## Problem

In the network shown, find the current in the  $10\ \Omega$  resistor.



Solution:

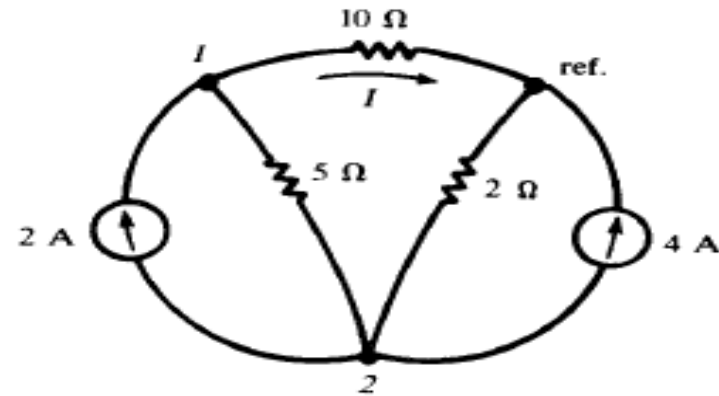

The nodal equations in matrix form are written by inspection.

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{10} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{1}{5} + \frac{1}{2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ -6 \end{bmatrix}$$

$$V_1 = \frac{\begin{vmatrix} 2 & -0.20 \\ -6 & 0.70 \end{vmatrix}}{\begin{vmatrix} 0.30 & -0.20 \\ -0.20 & 0.70 \end{vmatrix}} = 1.18 \text{ V}$$

Then,  $I = V_1/10 = 0.118 \text{ A}$ .





## Problem

Solve Problem by the node voltage method

